

Experiment 6

Basic Electronic circuits Filters using Op-Amps

1. Design a Low pass filter circuit having unity gain with $f_H=15.9\text{KHz}$.
 $R = 1\text{K}\Omega$ and $C = 0.01\mu\text{F}$.

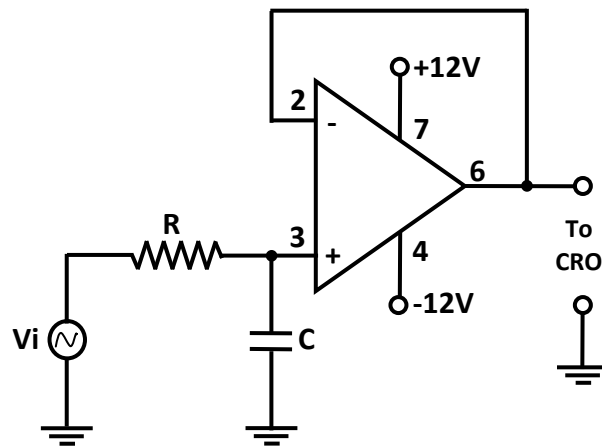


Fig 8.1: Low Pass Filter Circuit.

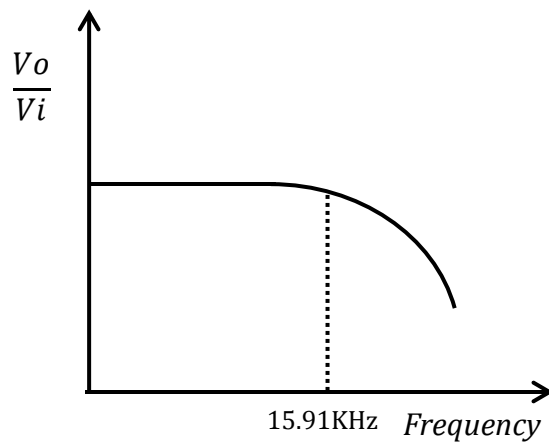


Fig 8.2 Model Graph for Low pass filter

$$f_H = \frac{1}{2\pi RC} = \frac{1}{2\pi * 1K * 0.01\mu} = 15.91\text{KHz}$$

Frequency (Hz)	Vin(v)	Vout(V)	Voltage Gain In dB $(20 \log_{10} \frac{V_o}{V_i})$
100			
200			
500			
1K			
1.5K			
2K			
5K			
10K			
12K			
15K			
20K			
50K			
100K			

2. Design a High Pass filter circuit having unity gain with $f_L=1.59\text{KHz}$.

$R = 1\text{K}\Omega$ and $C=0.1\mu\text{F}$

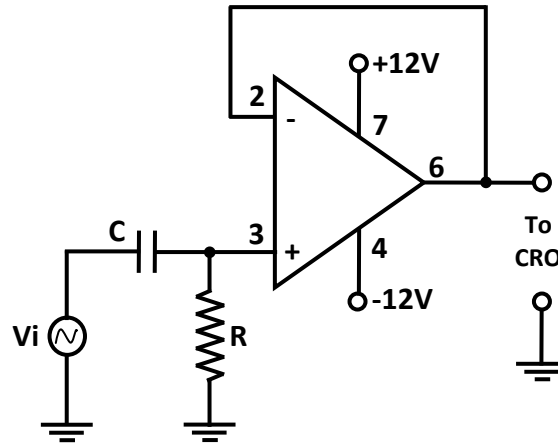


Fig 8.3: High Pass Filter Circuit.

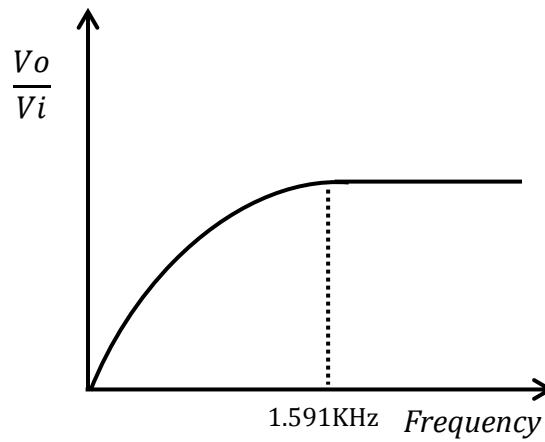


Fig 8.4: Model Graph for High pass filter

$$f_L = \frac{1}{2\pi RC} = \frac{1}{2\pi * 1K * 0.1\mu} = 1.591\text{KHz}$$

Frequency (Hz)	Vin(v)	Vout(V)	Voltage Gain In dB $20 \log_{10} \frac{V_o}{V_i}$
100			
200			
500			
1K			
1.5K			
2K			
5K			
10K			
12K			
15K			
20K			
50K			
100K			

3. Design a Band Pass filter circuit having unity gain with $f_L=1.59K$ Hz and $f_H = 15.9K$ Hz.

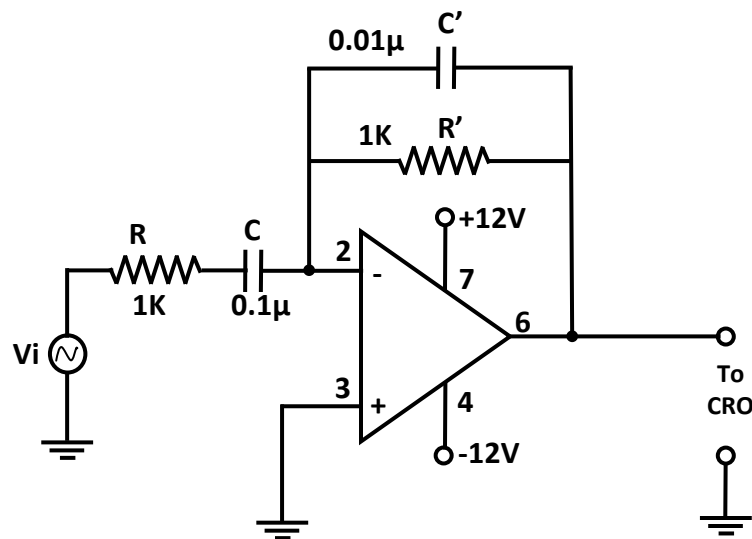


Fig 8.5: Band Pass Filter Circuit.

$$f_{c1} = \frac{1}{2\pi RC}$$

$$f_{c2} = \frac{1}{2\pi R' C'}$$

$$\text{Voltage Gain} = - \frac{R'}{R}$$

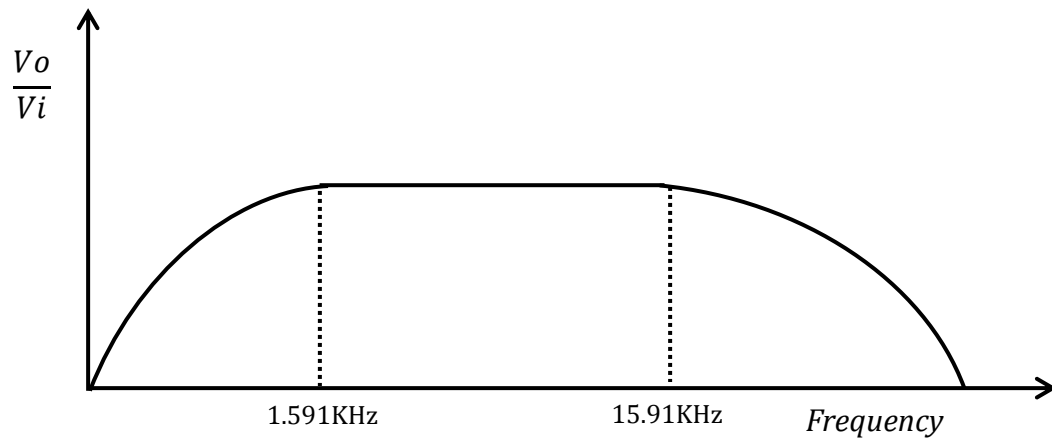


Fig 8.6: Model graph for Band Pass Filter

Frequency (Hz)	Vin(v)	Vout(V)	Voltage Gain In dB $20 \log_{10} \frac{V_o}{V_i}$
100			
200			
500			
1K			
1.5K			
2K			
5K			
10K			
12K			
15K			
20K			
50K			
100K			