

## Experiment 5

### Basic Electronics Circuits, IIIT Chittoor.

#### Design of waveform generators using Operational Amplifier

Aim: To design Sinusoidal, Triangular and Square waveform generators using op-amps for different frequencies and amplitudes and compare the experimental values with theoretical values.

##### A. Wein Bridge RC (Sinusoidal) Oscillator

1. The Wein bridge RC oscillator is shown in Fig. 6.1. Connect the circuit as shown in the Fig. 6.1 to generate a sinusoidal waveform with a frequency depends on the values. The expression for the frequency of the oscillator is given by Eqn. (6.1).

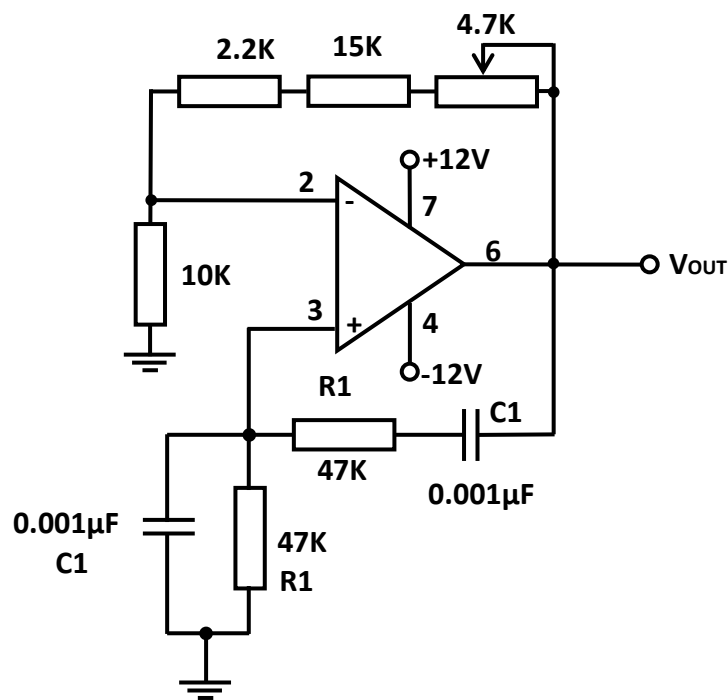


Fig 6.1 : Wein Bridge Oscillator

$$f = \frac{1}{2\pi R1 C1}$$

Eqn. (6.1)

## B. Square Waveform Generator

1. The square wave generator is shown in Fig. 6.2. Connect the circuit as shown in the Fig. 6.2 to generate a square waveform with a frequency depends on the RC values. The expression for the frequency of the square waveform is given by Eqn. (6.2).

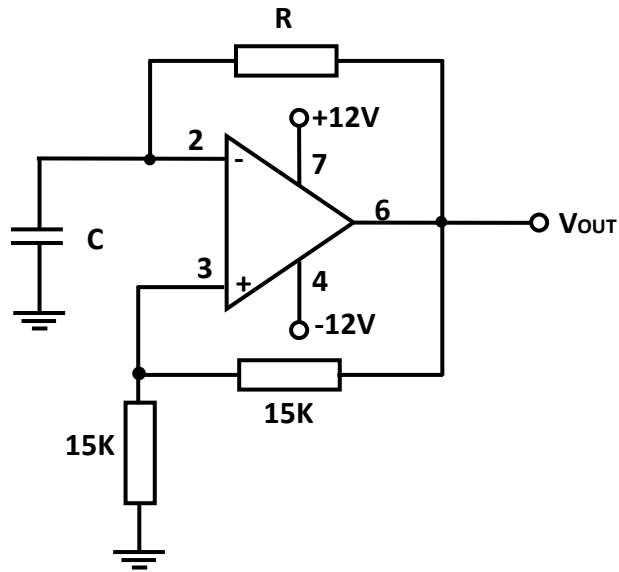


Fig 6.2 : Square Wave Generator

$$f = \frac{1}{2.19RC} \quad \text{Eqn. (6.2)}$$

### C. Triangular Waveform Generator

1. The triangular wave generator is shown in Fig. 6.3. Connect the circuit as shown in the Fig. 6.3 to generate a triangular waveform with a frequency depends on the values. The expression for the frequency of the triangular waveform is given by Eqn. (6.3).

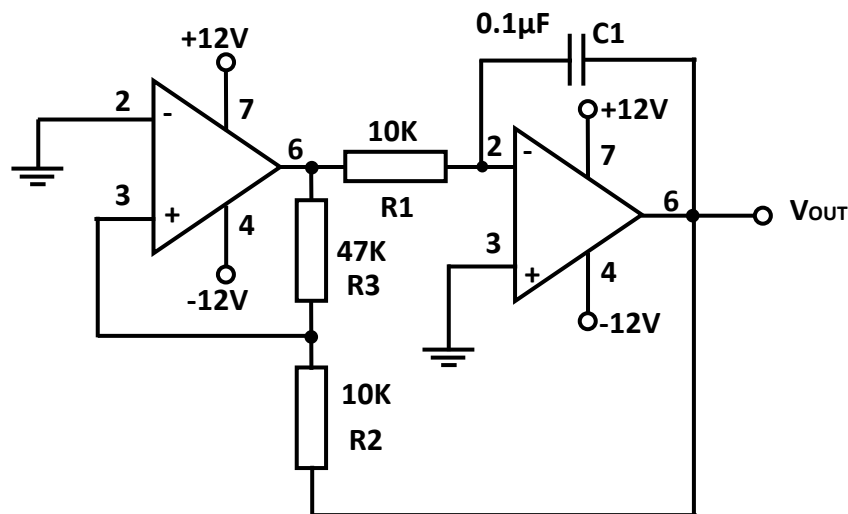


Fig 6.3 : Triangular Wave Generator

$$f = \frac{R3}{4R1C1R2} \quad \text{Eqn. (6.3)}$$

**Note: Plot all the waveforms on a graph sheet**