


CO: Computer Organization

Day3

Indian Institute of Information Technology, Sri City

Jan - May - 2018

<http://co-iiits.blogspot.in/>

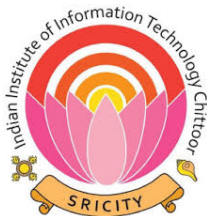

Arithmetic Operations on Integers


- ▶ Addition
 - ▶ Two 1-bit numbers
 - ▶ Two 4-bit numbers
 - ▶ Two 16-bit numbers
 - ▶ Two 64-bit numbers

Half Adder Truth Table

A	B	Carry(C)	Sum(S)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$\text{Sum}(S) = A \oplus B$$

$$\text{Carry}(C) = AB$$

 

If each gate delay is 1τ , S and C are available after 1τ .

Full Adder Truth Table

C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$$S = C_{in}^1(A \oplus B) + C_{in}(A \oplus B)^1 = C_{in} \oplus (A \oplus B)$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

Full Adder Circuit

$$S = C_{in}^1(A \oplus B) + C_{in}(A \oplus B)^1 = C_{in} \oplus (A \oplus B)$$

$$C_{out} = AB + C_{in}(A \oplus B)$$

 

if each gate delay is $1\mathcal{T}$, then S is available after $2\mathcal{T}$ and C_{out} is available after $3\mathcal{T}$.

Addition of two 4-bit numbers


Ripple Carry Adder

Input $A = A_3A_2A_1A_0$

Input $B = B_3B_2B_1B_0$


Carry $C = C_3C_2C_1C_0$ (initial carry)

Sum $S = C_4S_3S_2S_1S_0$

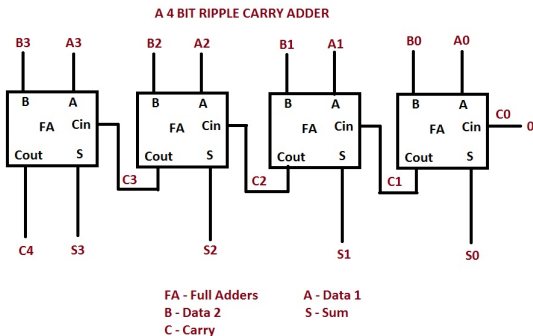

Addition of two 4-bit numbers

Ripple Carry Adder

 

Addition of two 4-bit numbers

Ripple Carry Adder

- ▶ C_1 is available after $3\mathcal{T}$.
- ▶ C_2 is available after $5\mathcal{T}$.
- ▶ C_3 is available after $7\mathcal{T}$.
- ▶ C_4 is available after $9\mathcal{T}$.

So the delay of 4-bit ripple carry adder is $9\mathcal{T}$.

Addition of two 4-bit numbers

Ripple Carry Adder

- ▶ C_1 is available after $3\mathcal{T}$.
- ▶ C_2 is available after $5\mathcal{T}$.
- ▶ C_3 is available after $7\mathcal{T}$.
- ▶ C_4 is available after $9\mathcal{T}$.

So the delay of 4-bit ripple carry adder is $9\mathcal{T}$.

Addition of two 4-bit numbers

Ripple Carry Adder

- ▶ C_1 is available after $3\mathcal{T}$.
- ▶ C_2 is available after $5\mathcal{T}$.
- ▶ C_3 is available after $7\mathcal{T}$.
- ▶ C_4 is available after $9\mathcal{T}$.

So the delay of 4-bit ripple carry adder is $9\mathcal{T}$.

Addition of two 4-bit numbers

Ripple Carry Adder

- ▶ C_1 is available after $3\mathcal{T}$.
- ▶ C_2 is available after $5\mathcal{T}$.
- ▶ C_3 is available after $7\mathcal{T}$.
- ▶ C_4 is available after $9\mathcal{T}$.

So the delay of 4-bit ripple carry adder is $9\mathcal{T}$.

Addition of two 4-bit numbers

Ripple Carry Adder

- ▶ C_1 is available after $3\mathcal{T}$.
- ▶ C_2 is available after $5\mathcal{T}$.
- ▶ C_3 is available after $7\mathcal{T}$.
- ▶ C_4 is available after $9\mathcal{T}$.

So the delay of 4-bit ripple carry adder is $9\mathcal{T}$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1T$.

Thereafter C_1, C_2, C_3, C_4 are available in $2T$.

Thereafter S_0, S_1, S_2, S_3 are available in $1T$.

\therefore Delay of CLA is $4T$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i . B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1\mathcal{T}$.

Thereafter C_1, C_2, C_3, C_4 are available in $2\mathcal{T}$.

Thereafter S_0, S_1, S_2, S_3 are available in $1\mathcal{T}$.

\therefore Delay of CLA is $4\mathcal{T}$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i \cdot B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1T$.

Thereafter C_1, C_2, C_3, C_4 are available in $2T$.

Thereafter S_0, S_1, S_2, S_3 are available in $1T$.

\therefore Delay of CLA is $4T$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i \cdot B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1T$.

Thereafter C_1, C_2, C_3, C_4 are available in $2T$.

Thereafter S_0, S_1, S_2, S_3 are available in $1T$.

\therefore Delay of CLA is $4T$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

$$\text{Let } G_i = A_i \cdot B_i \text{ and } P_i = A_i \oplus B_i$$

$$\text{then } S_i = C_i \oplus P_i$$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1T$.

Thereafter C_1, C_2, C_3, C_4 are available in $2T$.

Thereafter S_0, S_1, S_2, S_3 are available in $1T$.

\therefore Delay of CLA is $4T$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i . B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1\mathcal{T}$.

Thereafter C_1, C_2, C_3, C_4 are available in $2\mathcal{T}$.

Thereafter S_0, S_1, S_2, S_3 are available in $1\mathcal{T}$.

\therefore Delay of CLA is $4\mathcal{T}$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i . B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$

G_i and P_i are available after $1T$.

Thereafter C_1, C_2, C_3, C_4 are available in $2T$.

Thereafter S_0, S_1, S_2, S_3 are available in $1T$.

\therefore Delay of CLA is $4T$.

4-bit Adder

Carry Look Ahead Logic

$$S_i = C_i \oplus (A_i \oplus B_i)$$

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

Let $G_i = A_i . B_i$ and $P_i = A_i \oplus B_i$

then $S_i = C_i \oplus P_i$

$$C_{i+1} = G_i + C_i P_i$$

So the value of C_1, C_2, C_3, C_4 are:

$$C_1 = G_0 + C_0 P_0$$

$$C_2 = G_1 + C_1 P_1 = G_1 + G_0 P_1 + C_0 P_0 P_1$$

$$C_3 = G_2 + C_2 P_2 = G_2 + G_1 P_2 + C_1 P_1 P_2 = G_2 + G_1 P_2 + G_0 P_1 P_2 + C_0 P_0 P_1 P_2$$

$$C_4 = G_3 + C_3 P_3$$

$$= G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + C_0 P_0 P_1 P_2 P_3$$


G_i and P_i are available after $1\mathcal{T}$.

Thereafter C_1, C_2, C_3, C_4 are available in $2\mathcal{T}$.


Thereafter S_0, S_1, S_2, S_3 are available in $1\mathcal{T}$.

\therefore Delay of CLA is $4\mathcal{T}$.

Carry Look Ahead Circuit

 


4-bit Adder using CLA Logic

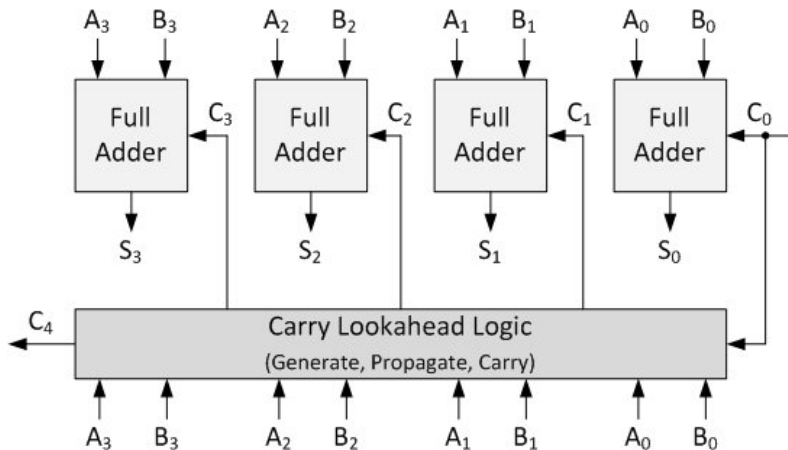

Think and Try


- 1 Speedup of 4-bit CLA adder as compared with 4-bit RCA(Ripple Carry Adder).
- 2 How to design a 16-bit adder using 4-bit RCAs.
- 3 How to design a 16-bit adder using 4-bit CLAs.
- 4 Latency of N-bit adder using L-bit CLAs.
- 5 How to design a 64-bit adder using 16-bit adders. The 16-bit adders are designed using 4-bit CLAs.

A 4-bit adder or subtractor

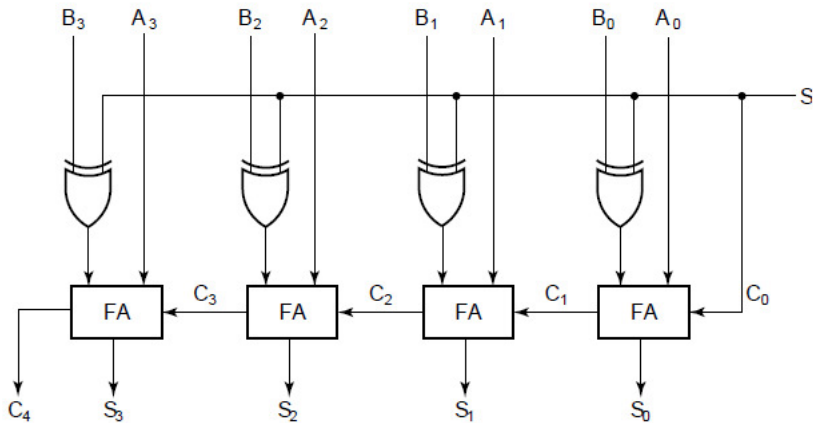

Write equations for Carry(C) and Overflow detection.

A 4-bit adder or subtractor

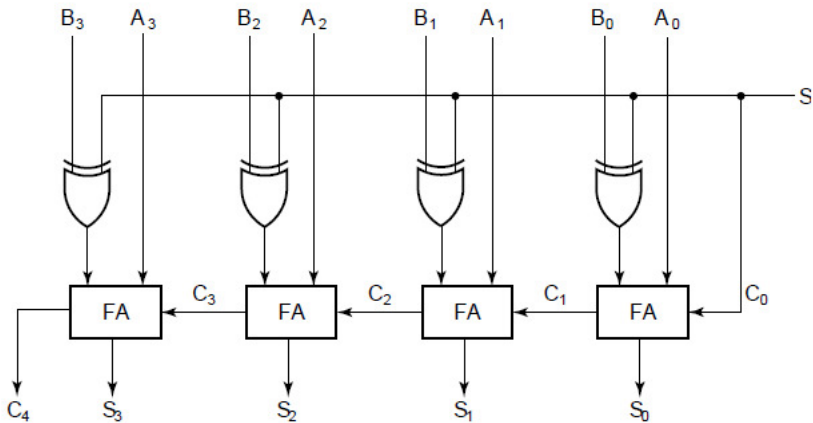

Write equations for Carry(C) and Overflow detection.