


CO: Computer Organization

Tutorial-2

Indian Institute of Information Technology, Sri City

Jan - May - 2018

<http://co-iiits.blogspot.in/>

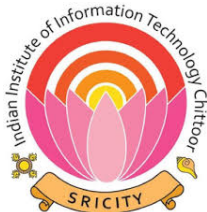

Tutorial -2

- 1 Consider two n-bit numbers in 2's complement form. Show that the logic expression $C_n \oplus C_{n-1}$ is a correct indicator for overflow detection. Where C_n is final carry.
- 2 Design an efficient 64-bit adder using 8-bit CLAs.