

**Characteristics of BJT transistor in common emitter configuration**

The basic circuit diagram for studying characteristics of BJT is shown in the Fig. 3.1. The input voltage is applied between base and emitter terminals and the output voltage is measured between collector and emitter terminals. Here emitter region of the transistor is common to both input and output and hence the name common emitter configuration. While performing the experiment do not exceed the ratings of the transistor. This may lead to damage the transistor. Connect voltmeter and ammeter or multimeters with correct polarities as shown in the circuit diagram

**Input characteristics** are obtained between the input current and input voltage keeping the output voltage ( $V_{CE}$ ) constant.

1. Connect the circuit as shown in Fig 3.1
2. Keep output voltage  $V_{CE} = 0$  V by varying  $V_{CC}$ .
3. Varying  $V_{BB}$  gradually, note down base current  $I_B$  and base-emitter voltage  $V_{BE}$ .
4. Vary in steps of 0.1 V from 0 V to 1.2 V.
5. Repeat above procedure (step 3) for  $V_{CE} = 5$  V. Tabulate readings in Table 3.1
6. Plot the graph between  $V_{BE}$  and  $I_B$  for constant  $V_{CE}$  values.

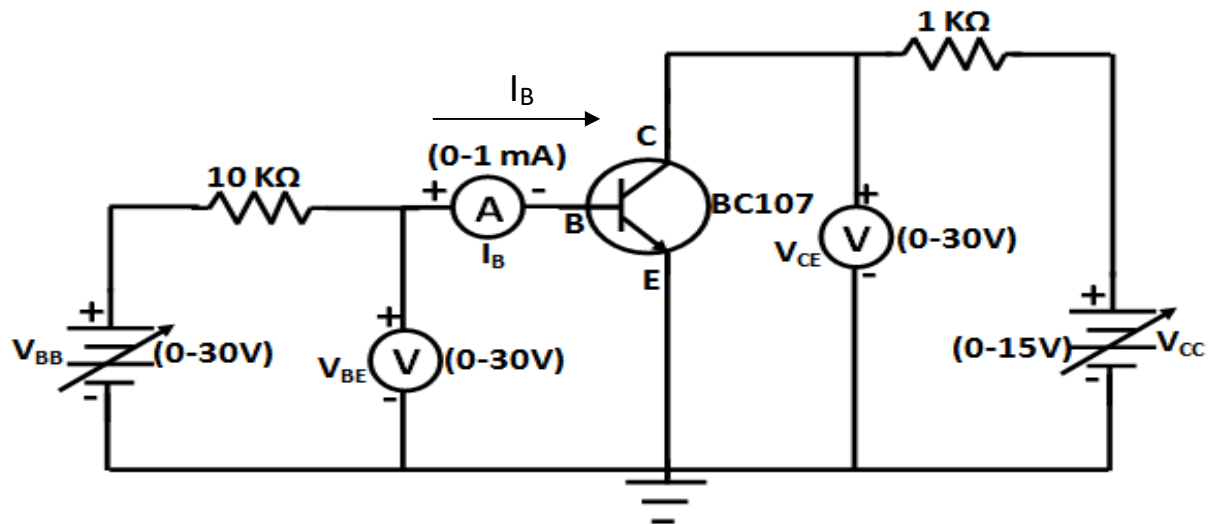


Fig. 3.1: Circuit for plotting input characteristics of BJT in CE configuration

$V_{CE} = 0V$		$V_{CE} = 5V$	
$V_{BE} (V)$	$I_B (\mu A)$	$V_{BE} (V)$	$I_B (\mu A)$

Table 3.1: Experimental data for  $V_{BE}$  vs.  $I_B$  for different values of  $V_{CE}$

To obtain input resistance find  $\Delta V_{BE}$  and  $\Delta I_B$  for a constant  $V_{CE}$  on one of the input characteristic

$$\text{Input impedance} = h_{ie} = R_i = \frac{\Delta V_{BE}}{\Delta I_B} \quad (V_{CE} \text{ is constant}) =$$

$$\text{Reverse voltage gain} = h_{re} = \frac{\Delta V_{BE}}{\Delta V_{CE}} \quad (I_B = \text{constant}) =$$

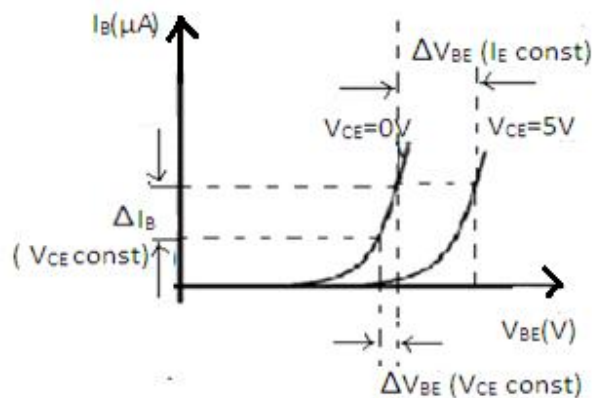


Fig. 3.2: Input characteristics of BJT in CE configuration

**Output characteristics** are plotted between the output voltage ( $V_{CE}$ ) and output current ( $I_C$ ) at constant input current.

1. Connect the circuit as shown in the Fig 3.3.
2. Keep base current  $I_B = 20 \mu A$  by varying  $V_{BB}$ .
3. Varying  $V_{CC}$  gradually in steps of 1V up to 12V and note down collector current  $I_C$  and Collector-Emitter Voltage ( $V_{CE}$ ).
4. Repeat above procedure (step 3) for  $I_B = 20 \mu A, 40 \mu A, 60 \mu A$ . Tabulate readings in Table 3.2
5. Plot the graph between  $V_{CE}$  and  $I_C$  for different values of  $I_B$ .

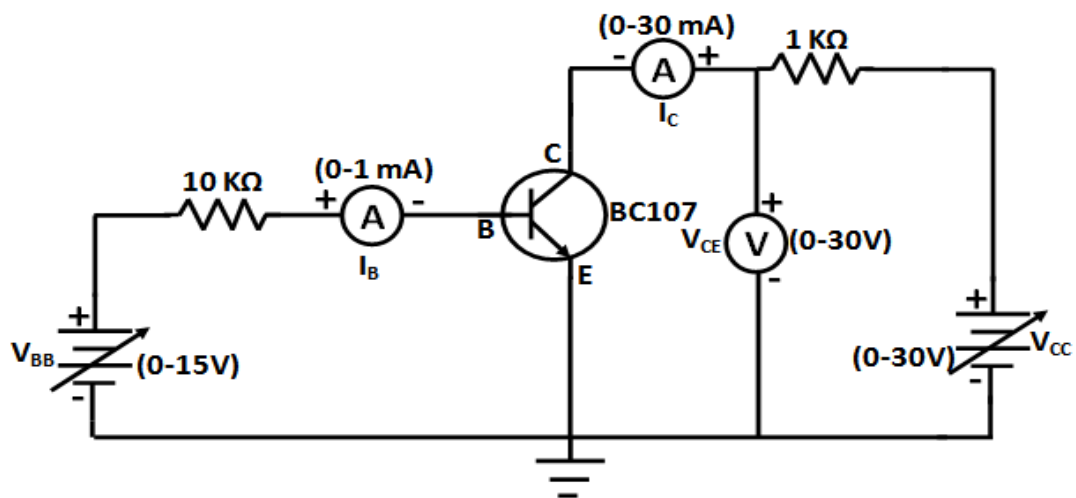


Fig 3.3: Circuit for plotting input characteristics of BJT in CE configuration

$V_{BB}(\text{Volts})$	$I_B = 20\mu\text{A}$		$I_B = 40\mu\text{A}$		$I_B = 60\mu\text{A}$	
	$V_{CE}(\text{V})$	$I_C(\text{mA})$	$V_{CE}(\text{V})$	$I_C(\text{mA})$	$V_{CE}(\text{V})$	$I_C(\text{mA})$

Table 3.2: Experimental data for  $V_{CE}$  vs.  $I_C$  for different values of  $I_B$

To obtain output resistance find  $\Delta I_C$  and  $\Delta V_{CB}$  at a constant  $I_B$  on one of the output characteristics

Output admittance  $\frac{1}{h_{oe}} = R_o = \frac{\Delta I_C}{\Delta V_{CE}} \quad (I_B \text{ is constant}) =$

Forward current gain  $= h_{fe} = \frac{\Delta I_C}{\Delta I_B} \quad (V_{CE} = \text{constant}) =$

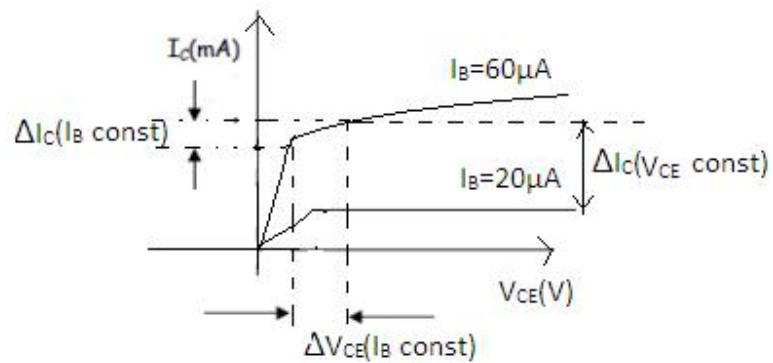


Fig. 3.4: output characteristics of BJT in CE configuration

### **Observations:**

1. Comment on the nature of input characteristics
2. What is the range of input and output resistances of a BJT working in CE mode
3. What is the current gain of the transistor