


Assignment 1A

BEC, IIITS

Nodal analysis

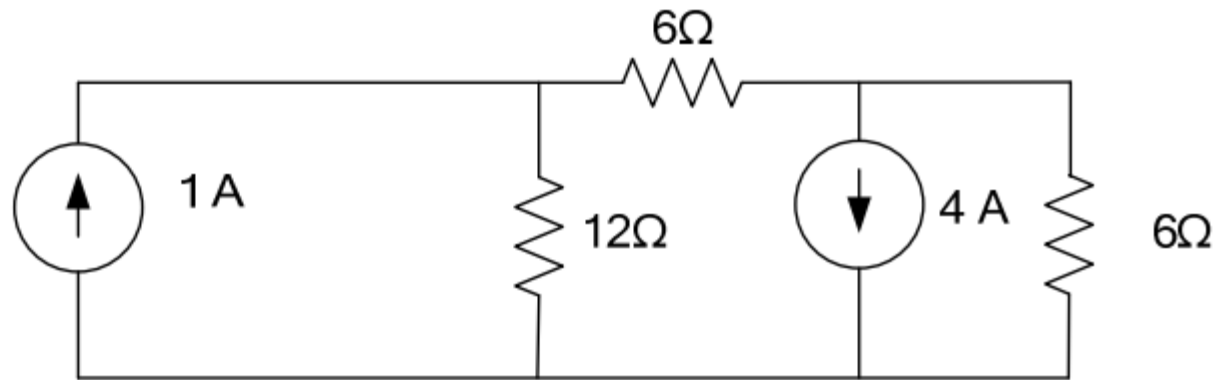
- Problem 1

Find the node voltages of the following circuit.




$$V_1 = -6V$$
$$V_2 = -15V$$

- Assign voltages

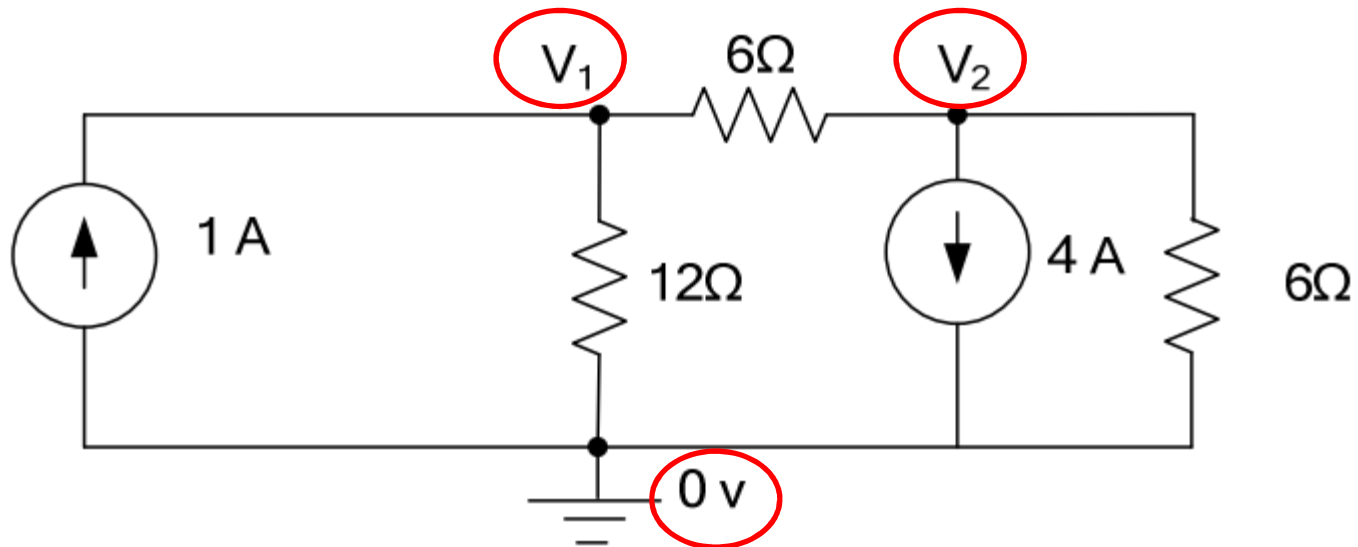


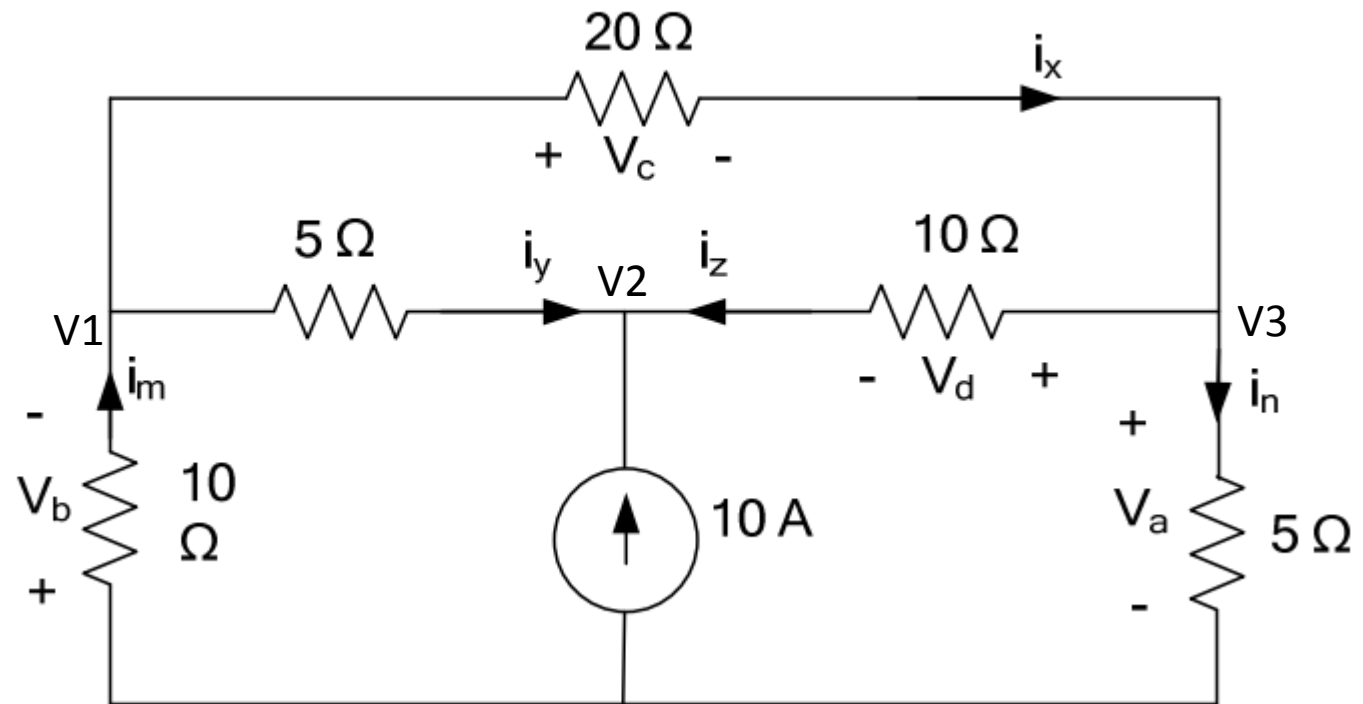- Problem 2

Use the nodal analysis to find the $i_x, i_y, i_z, i_n, i_m, V_a, V_b, V_c, V_d$.




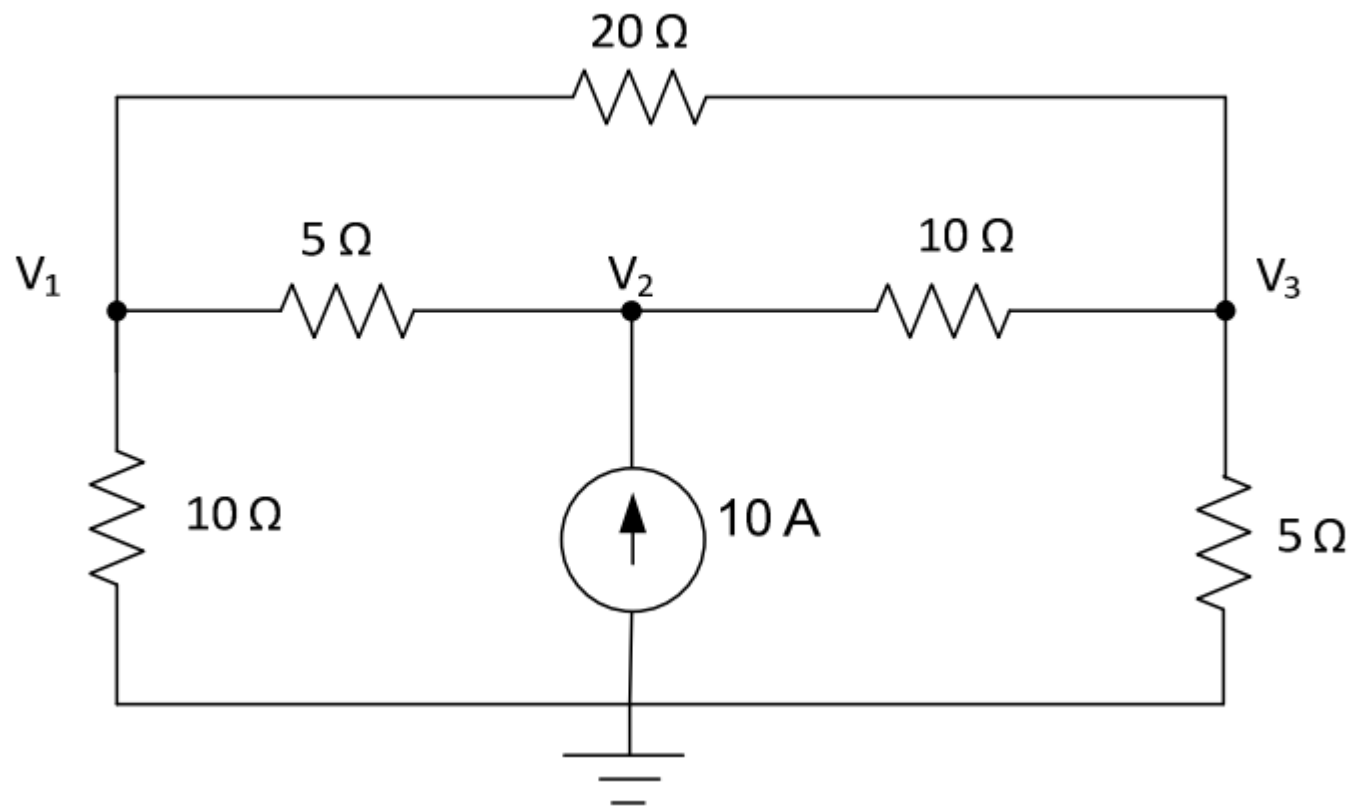Assign voltages variable to all nodes except the reference node.




- Problem 3

Find i_0 by using the nodal analysis:

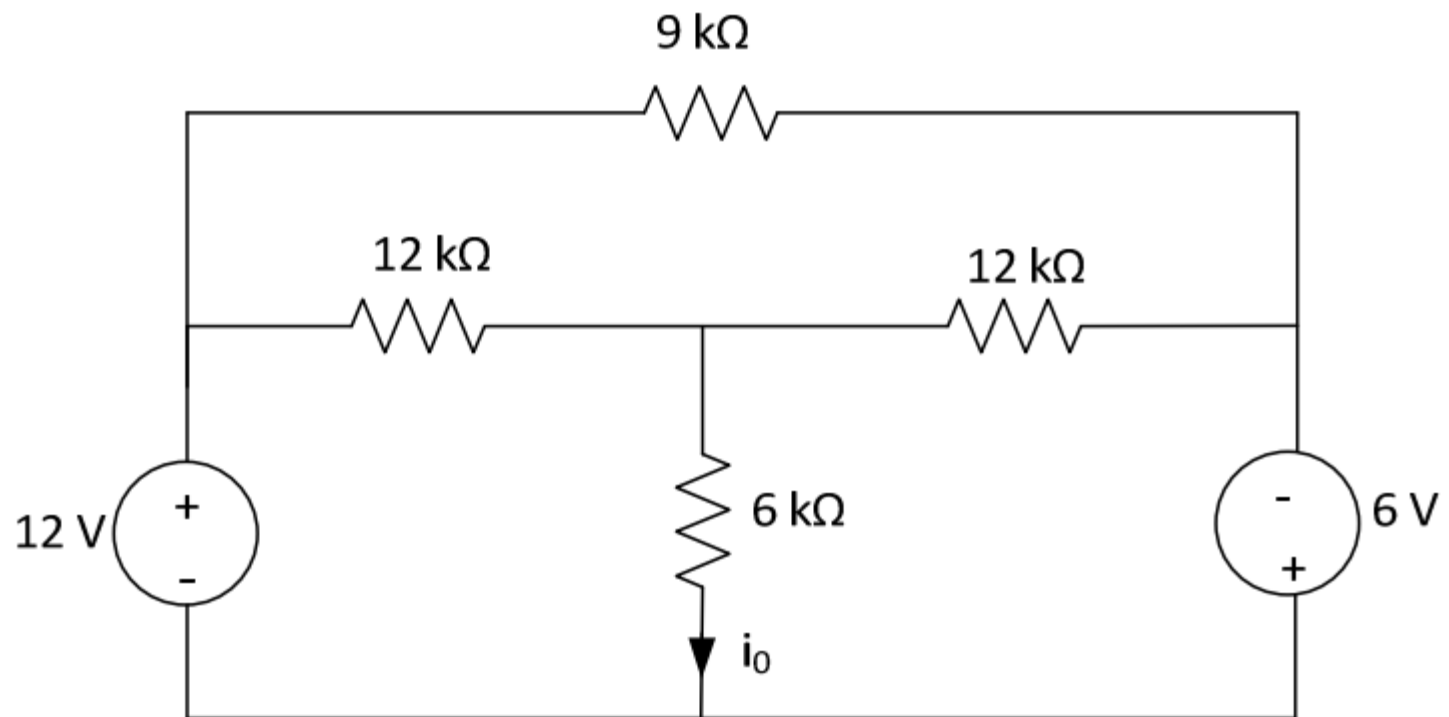


Find node voltages

- Problem 4

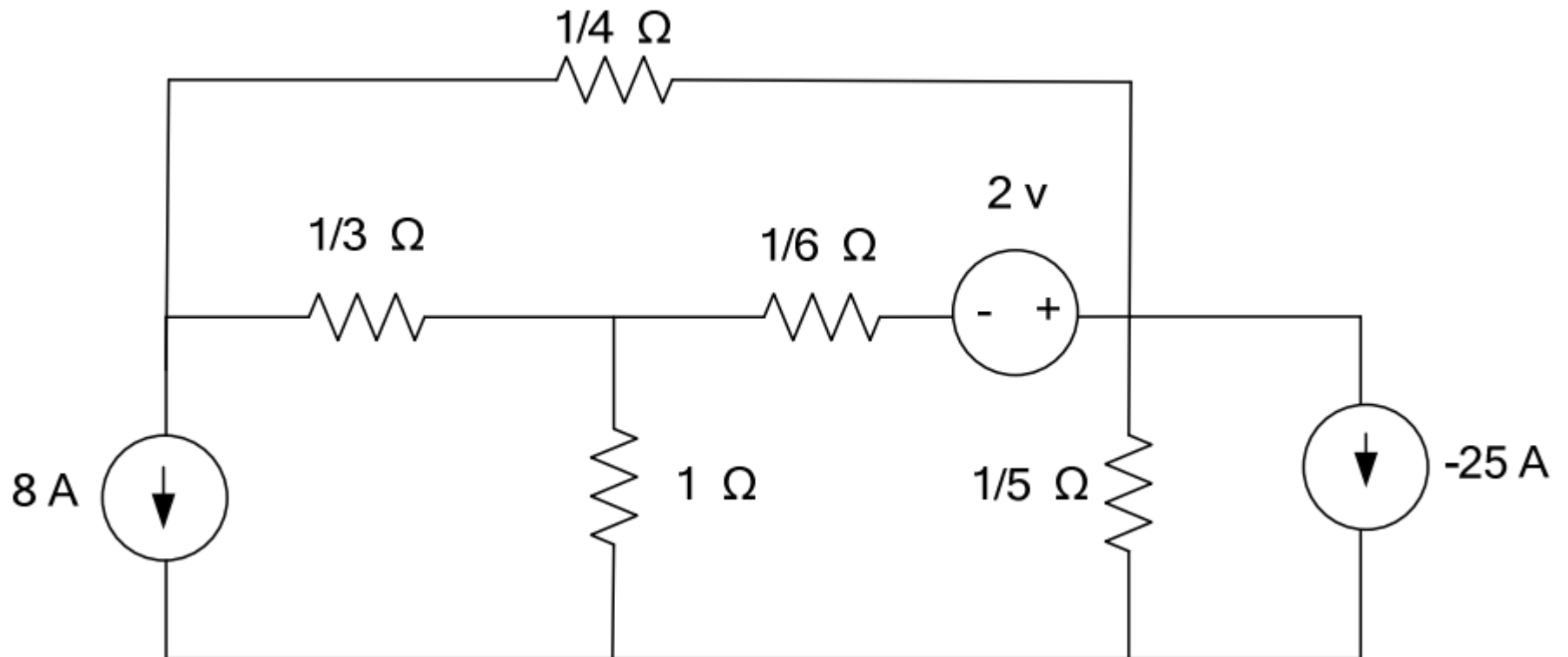


Problem on dependent source

- Problem 5

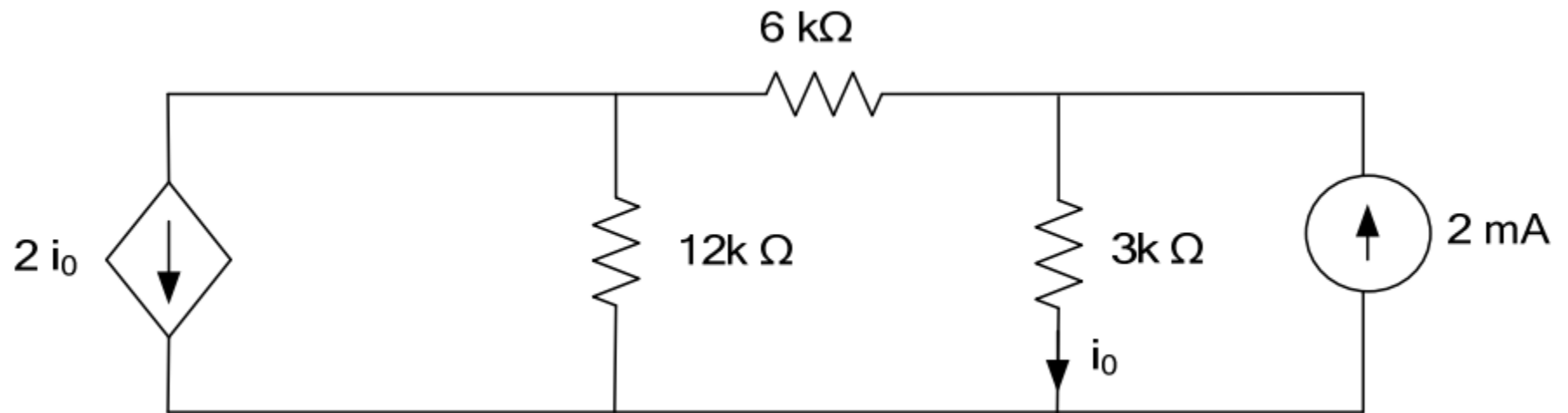

Find node voltages and currents

- Problem 6

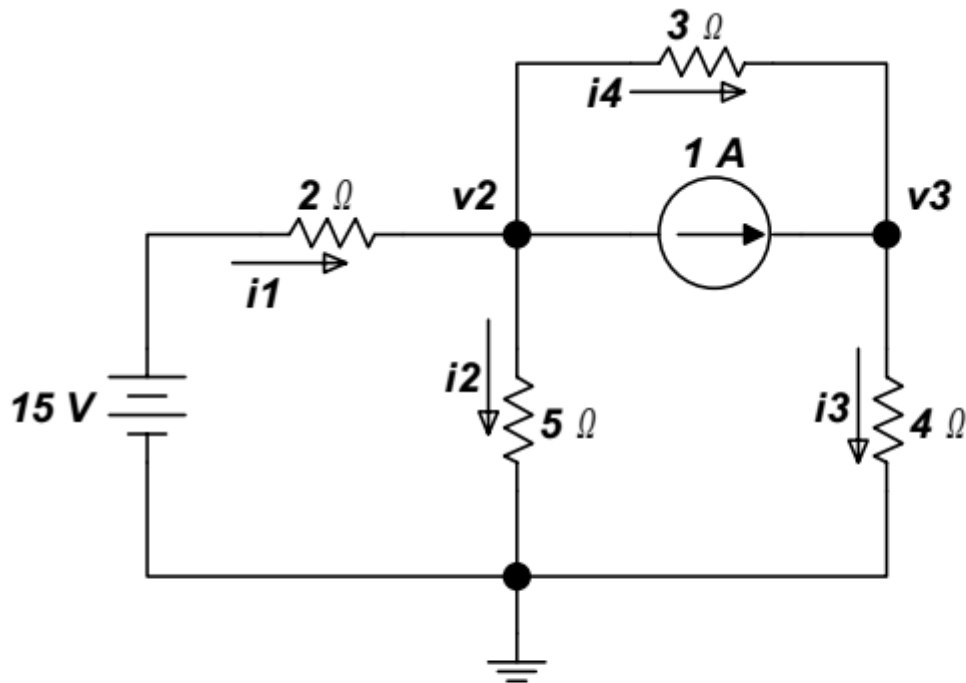

Answer: $i_1 = 3.31\text{A}$, $i_2 = 1.68\text{A}$, $i_3 = 1.63\text{A}$, $i_4 = 0.627\text{A}$, $v_2 = 8.39\text{V}$, $v_3 = 6.51\text{V}$