

# **Operational Amplifier**

Dr. E. Paul Brineard

# Unit 2

- **Op-Amp (operational amplifier):** Amplifier parameters, controlled source models, classification, the operational amplifier (OP-AMP) as a linear active device, the VCVS model of an op-amp, different amplifier configurations using op-amp (open loop-closed loop), frequency response of op-amp and op-amp based amplifiers. Calculation of CMRR, Gain Band width product. Op-Amp as integrator, differentiator, addition, subtraction etc.


# Op-amp

- Direct coupled very high gain voltage amplifier
- Integrated circuit
- Differential input and single output

Direct coupled: the output of one stage of amplifier is connected directly to the input of next stage without any coupling capacitor
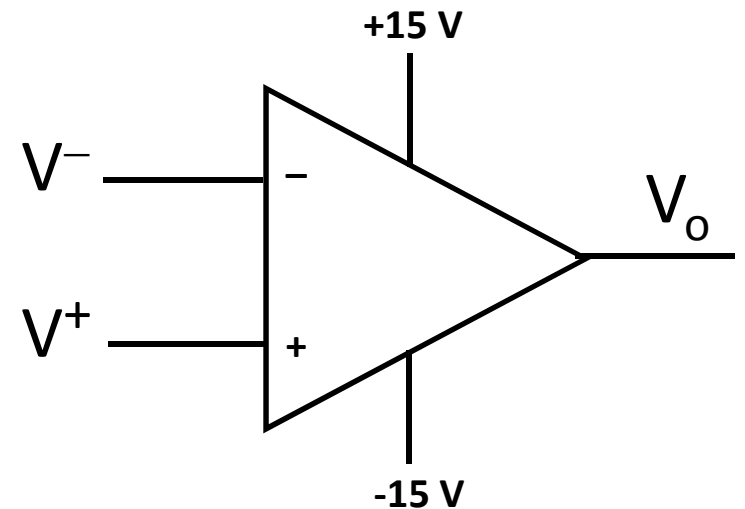
# Ideal characteristics of op-amp

- Open loop gain infinite,  
 $A_{OL} = \infty$
- Input impedance infinite,  
 $R_i = \infty$
- Output impedance low,  
 $R_o = 0$
- Bandwidth infinite,  
 $BW = \infty$
- Zero offset, ie,  $V_o = 0$  when  
 $V^+ = V^- = 0$



Op-amp circuit symbol

# Operational characteristics of op-amp

- Practical op-amp
  - Draws current
  - Inputs respond differently to currents and voltages due to mismatches in transistors
  - Operating point shifts with temperature
- Add error to the DC output voltage

# DC non-ideal characteristics of op-amp

- Input bias current
- Input offset current
- Input offset voltage
- Thermal drift

# Differential and Common-Mode Signals


# CMRR

- Common mode rejection ratio



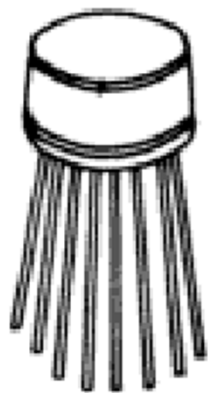
# Packages of IC741


Metal can (TO) package, Dual-in-line package, Flat package



TO-5 style package  
with straight leads


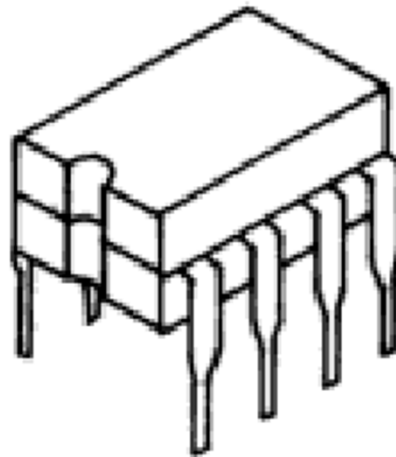


Ceramic flat package

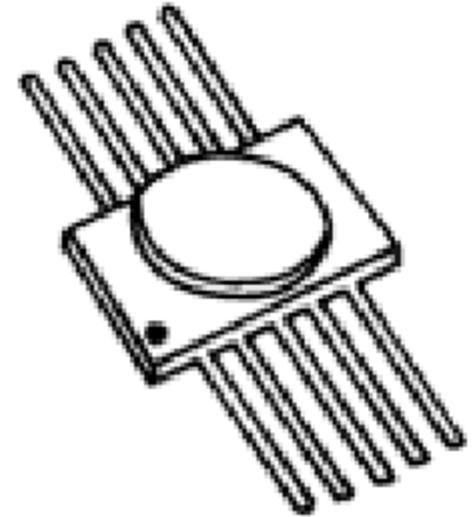

IC packages of  $\mu A741$


# Pin diagram of 741 op-amp

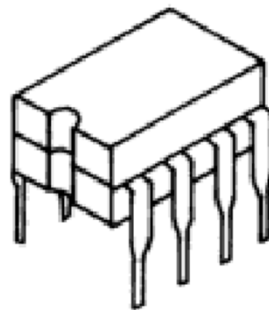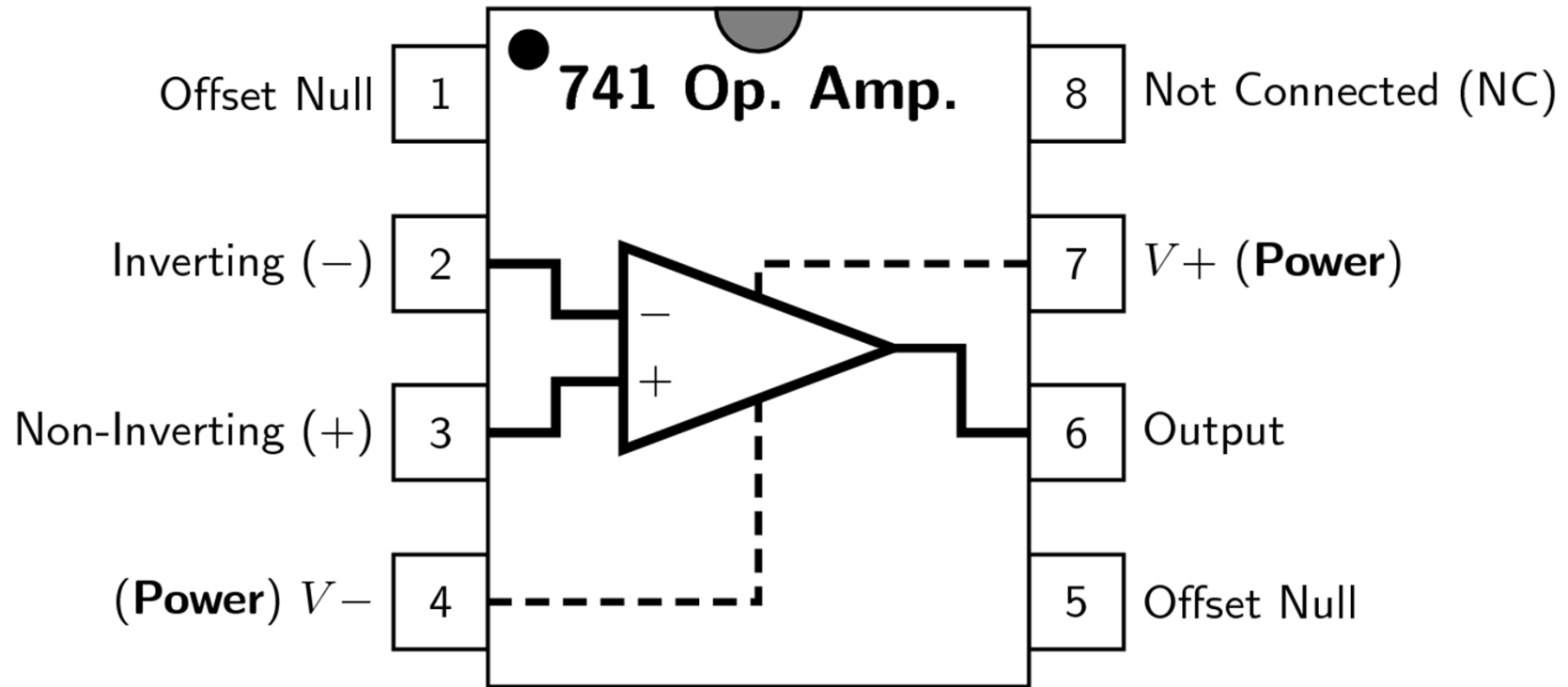

Dual-in-line package
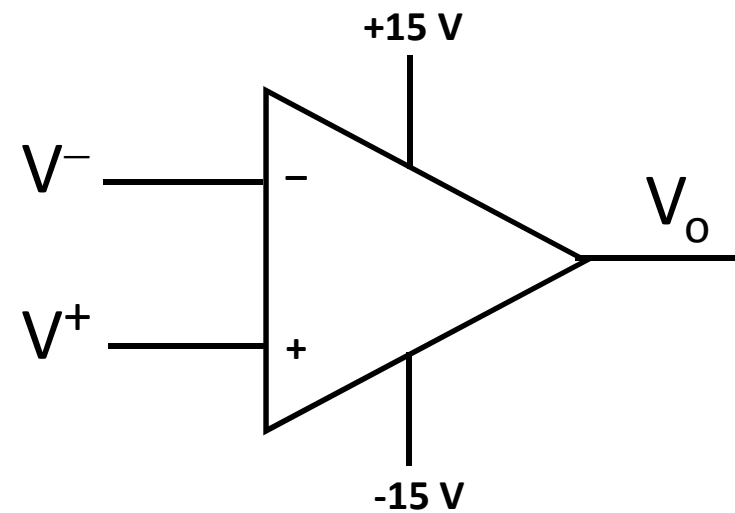
# Op-amp terminals

- Primarily
  - Two input terminals
    - Inverting terminal ( $V^-$ )
    - Non-inverting terminal ( $V^+$ )
  - One output terminal
  - Two terminals for power supply



Op-amp circuit symbol


# Op-amp manufacturers

<b>Manufacturer</b>	<b>Product number</b>
Fairchild (Original)	$\mu$ A741
National semiconductor	LM741
Motorola	MC1741
RCA	CA3741
Texas instruments	SN52741
Signetics	N5741


# Op-amp classes

Class	Application	
741	Military grade op-amp (Operating temp. range -55 °C to 125 °C)	
741C	Commercial grade op-amp (Operating temp. range 0 °C to 70/75 °C)	
741A	Improved version of 741	Better electrical specifications
741E	Improved version of 741 C	
741S	Military grade op-amp with higher slew-rate	
741SC	Commercial grade op-amp with higher slew-rate	

# Internal circuit diagram of 741

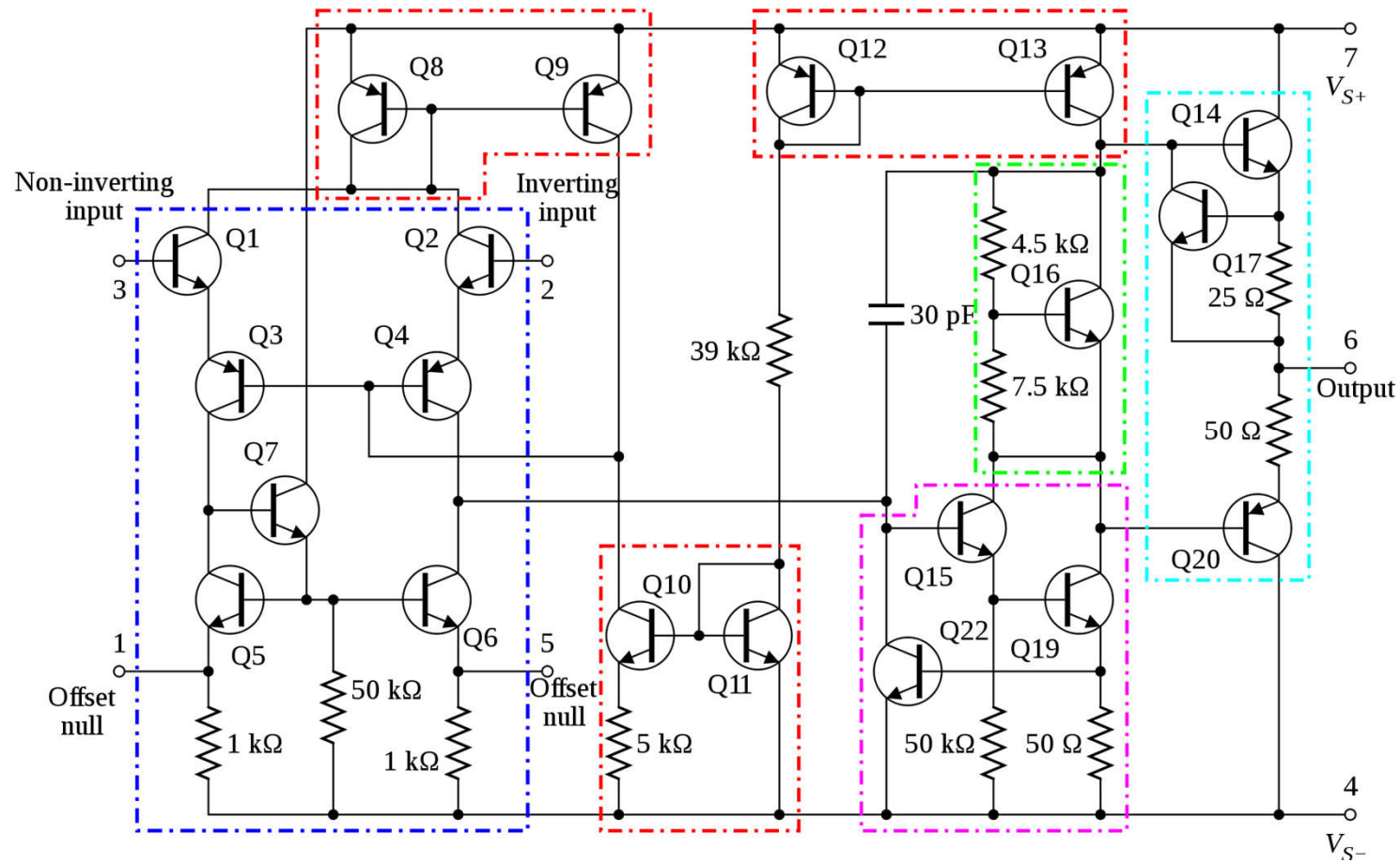


# Block diagram of op-amp

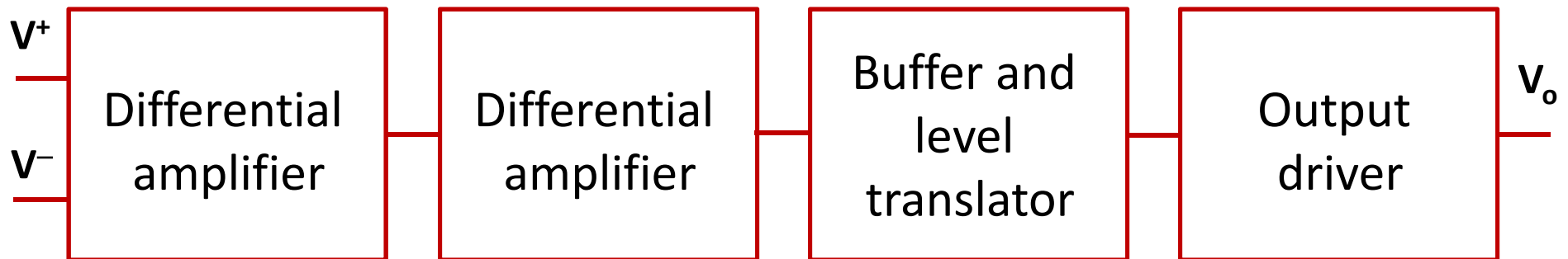

- First two stages, cascaded differential amplifier
  - High gain, high resistance


# Block diagram of op-amp

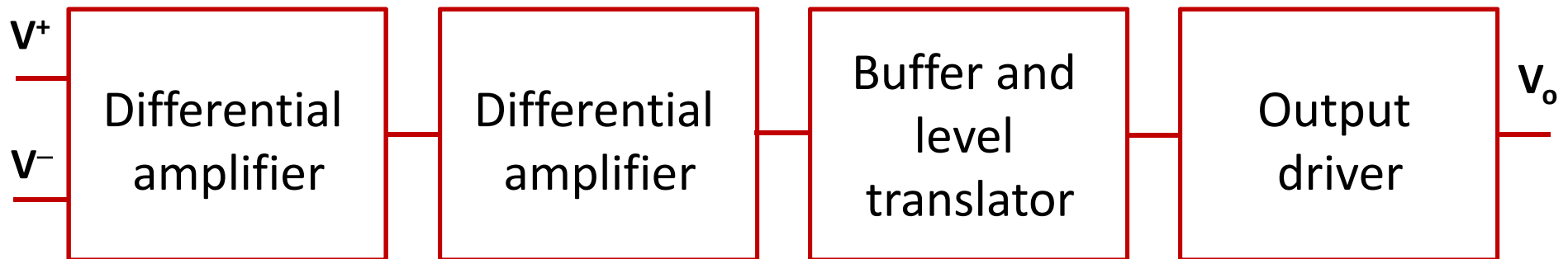

- Buffer
  - Emitter follower
  - Very high input impedance, to prevent loading to the amplifier
- Level shifter
  - Adjusts DC voltages so that output voltage is zero for zero input voltage



# Block diagram of op-amp

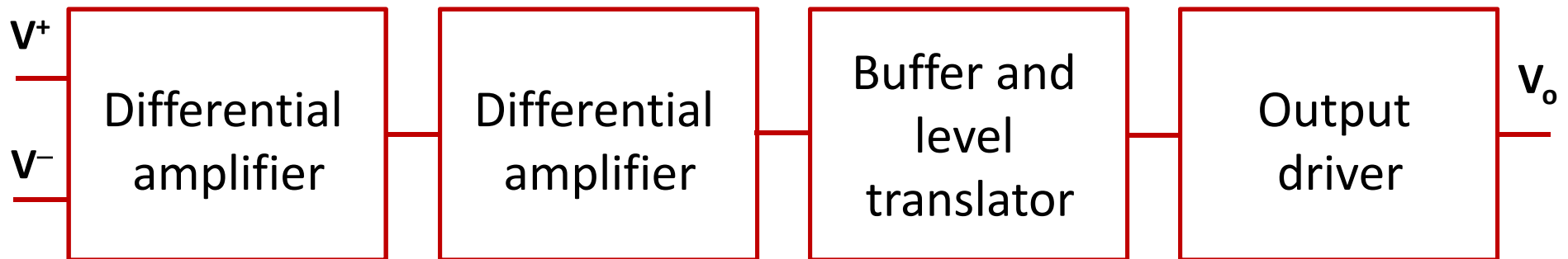


- Output stage
  - To provide low output impedance

# Differential amplifier

- Provide high gain to the difference-mode signal
- Cancel common-mode signal


# Block diagram of op-amp

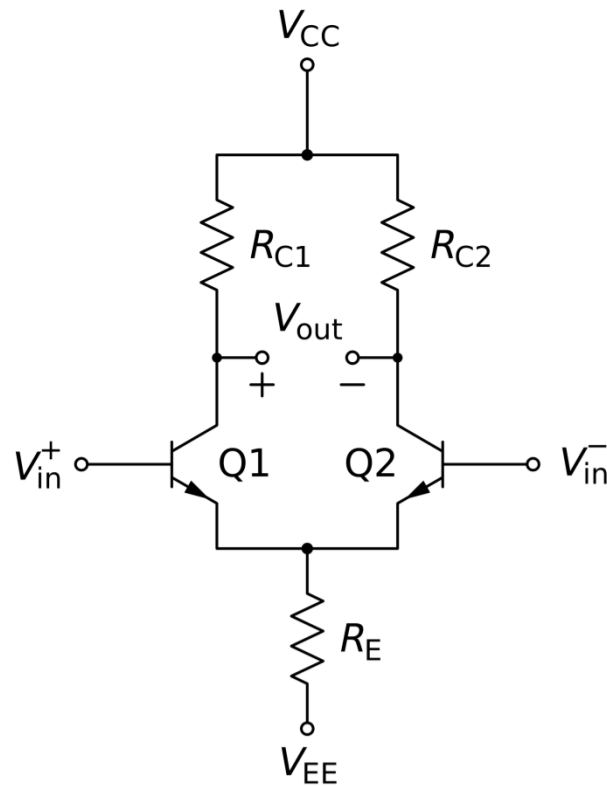
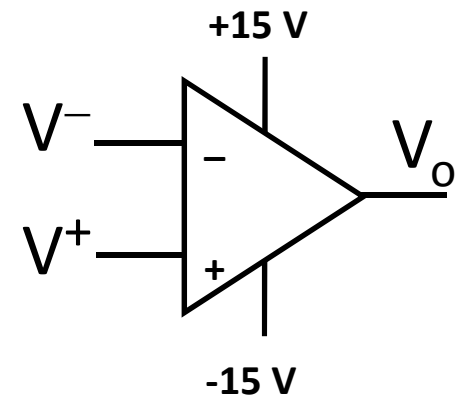
# Operations of op-amp

- **Open loop**


- Output is driven into saturation
- Comparator
- Zero crossing detector




---

- **Closed loop**

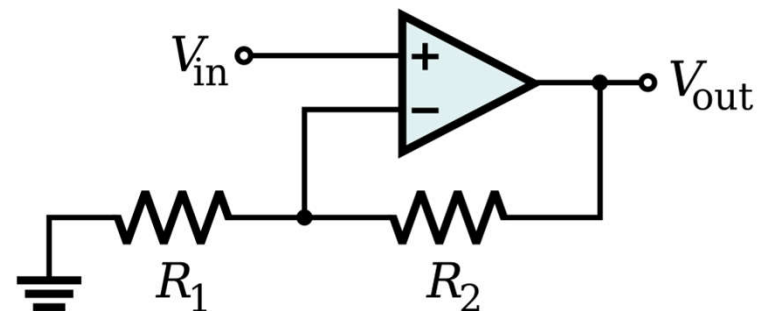- Negative feed back
- Linear output range



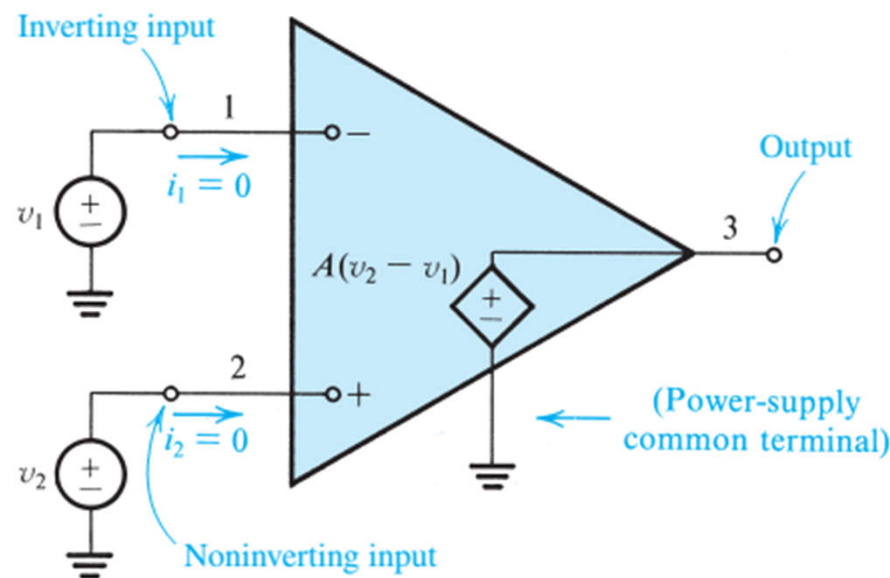
# Equivalent circuit of the ideal op-amp (VCVS model of op-amp)



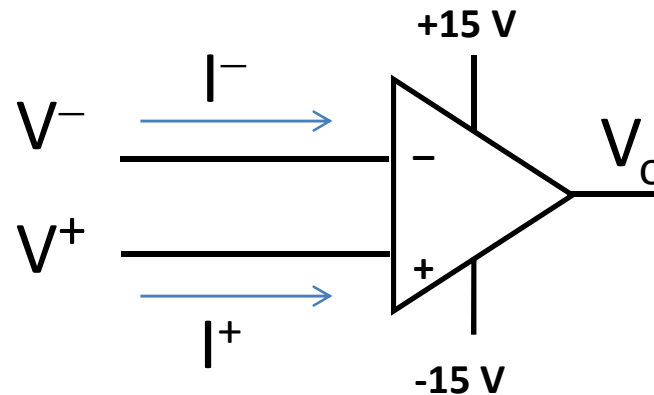
# Analysis of op-amp

- Assumptions
  - Current entering the op-amp terminals is zero,  $I^+ = I^- = 0$
  - Difference voltage is zero,  $V^+ - V^- = 0$



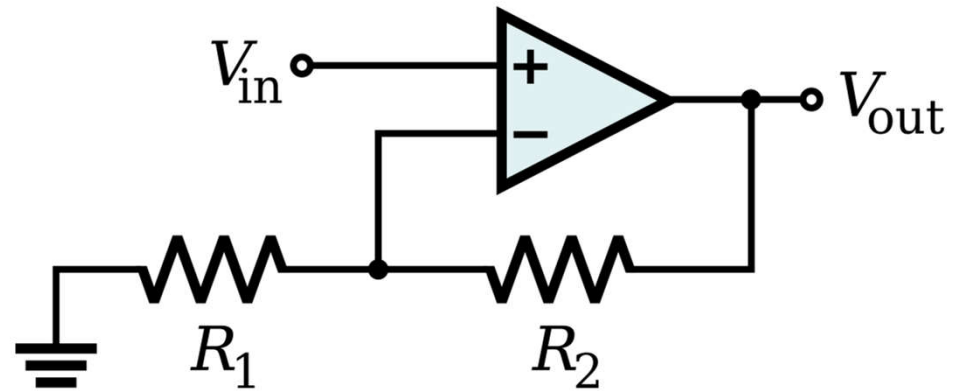
# Non-inverting op-amp


$$i_1 = i_2$$
$$\frac{0 - V_{in}}{R_1} = \frac{V_{in} - V_{out}}{R_2}$$


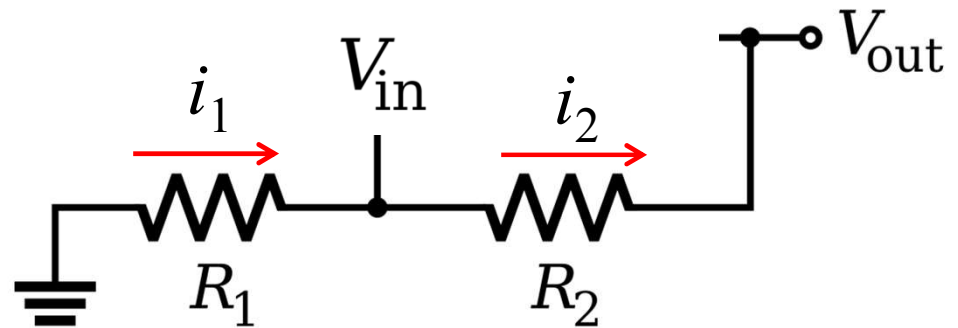
$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$




Q: why do you require  $R_1$

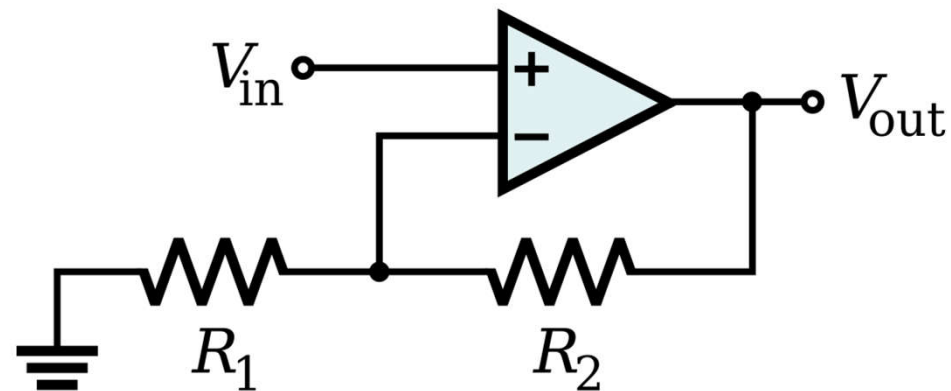




# Inverting op-amp

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

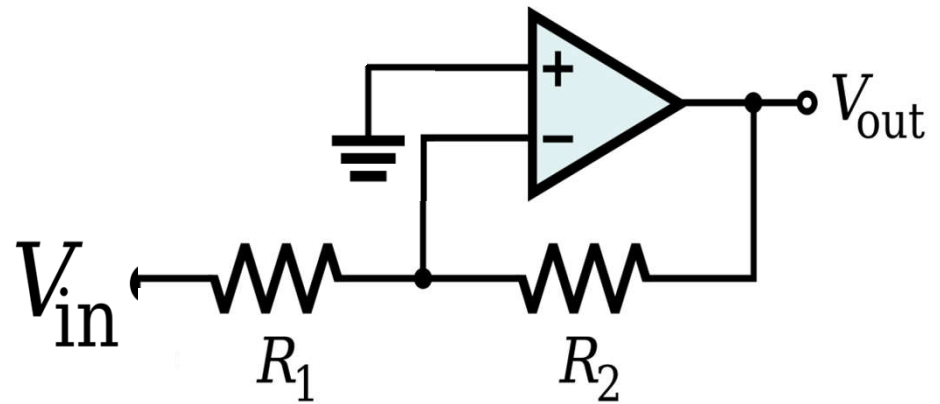


# Inverting summing amplifier

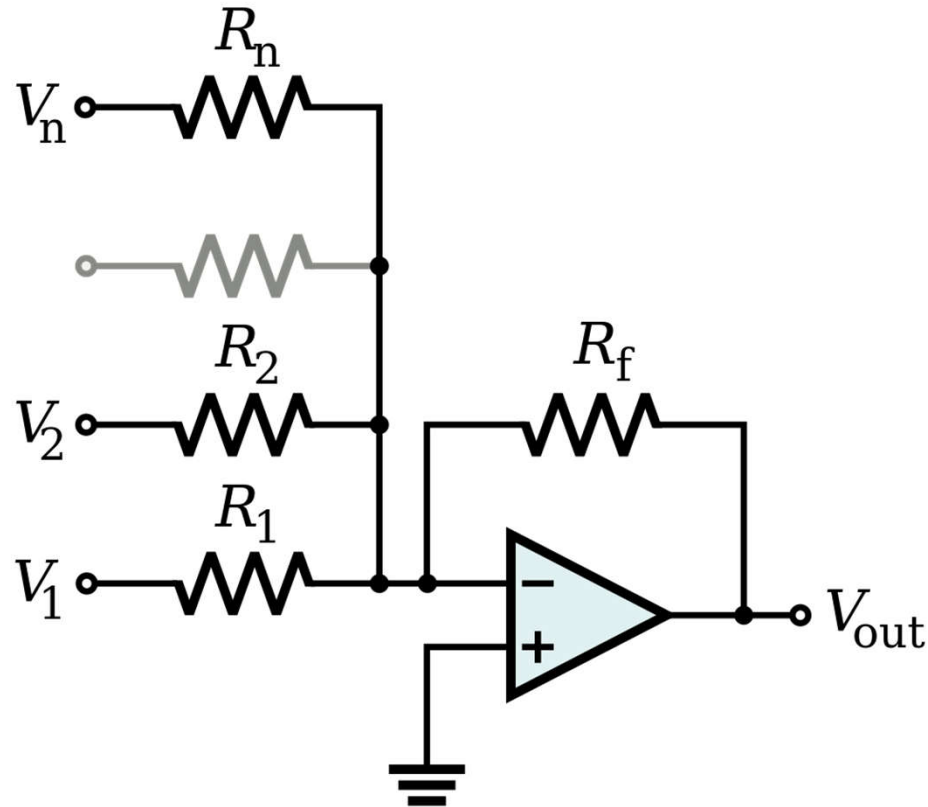


$$V_{out} = - \left( \frac{R_f}{R_1} + \frac{R_f}{R_2} + \dots + \frac{R_f}{R_n} \right) V_{in}$$

# Difference amplifier

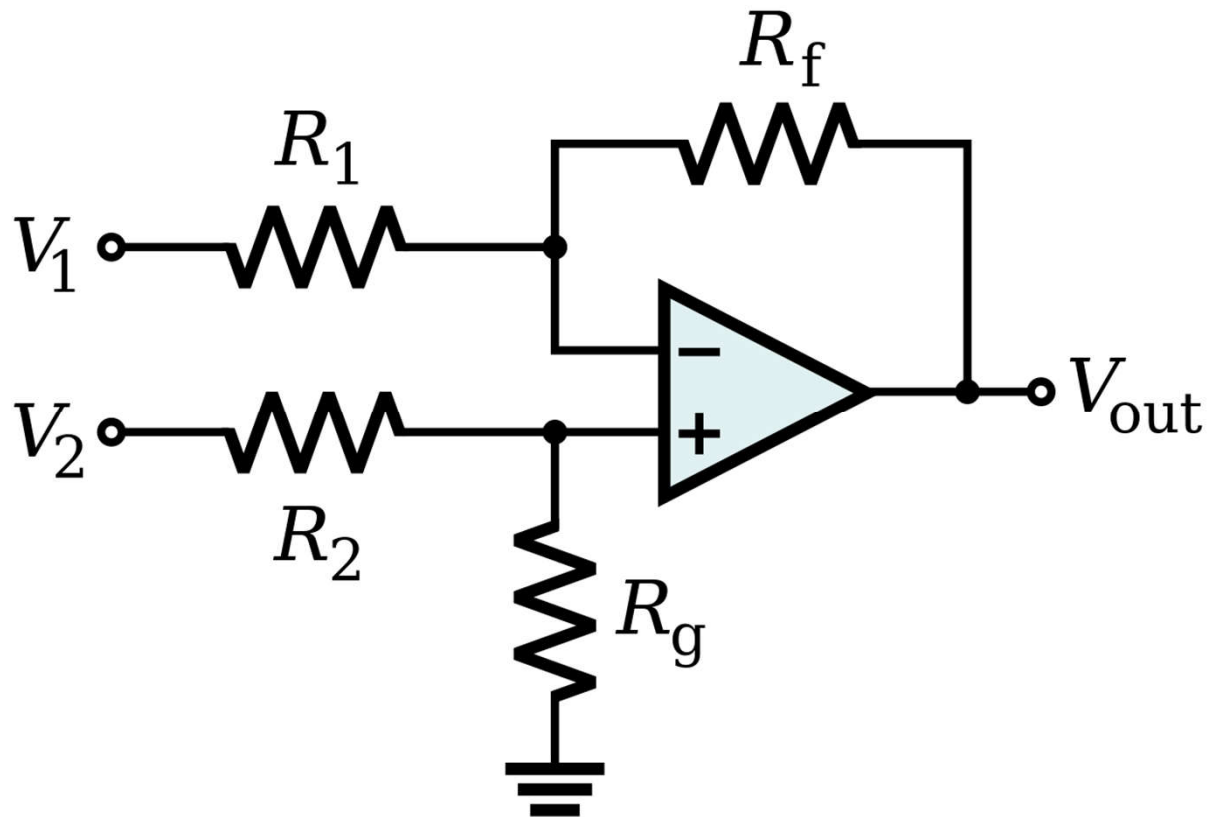

# Instrumentation amplifier

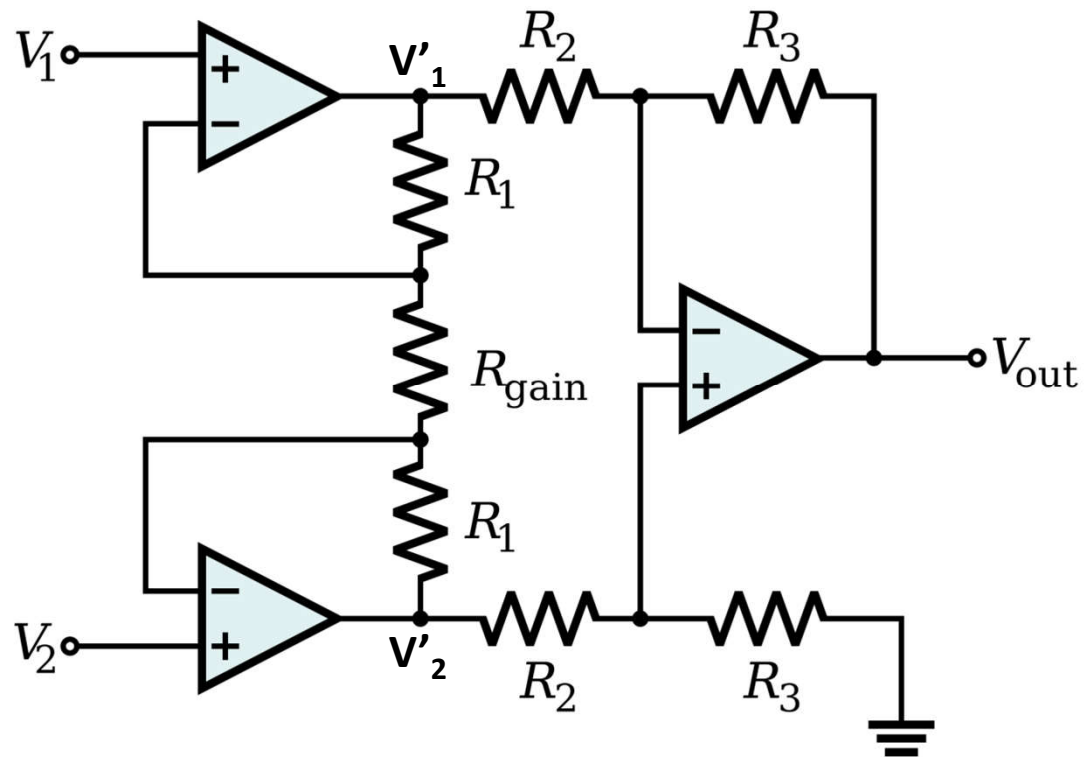


$$V_{out} = \left( 1 + \frac{2R_1}{R_{gain}} \right) \left( \frac{R_3}{R_2} \right) [V_2 - V_1]$$


# Problem: Superposition theorem

- Use the superposition principle to find the output voltage of the circuit shown in Fig.

$$v_o = 6v_1 + 4v_2$$

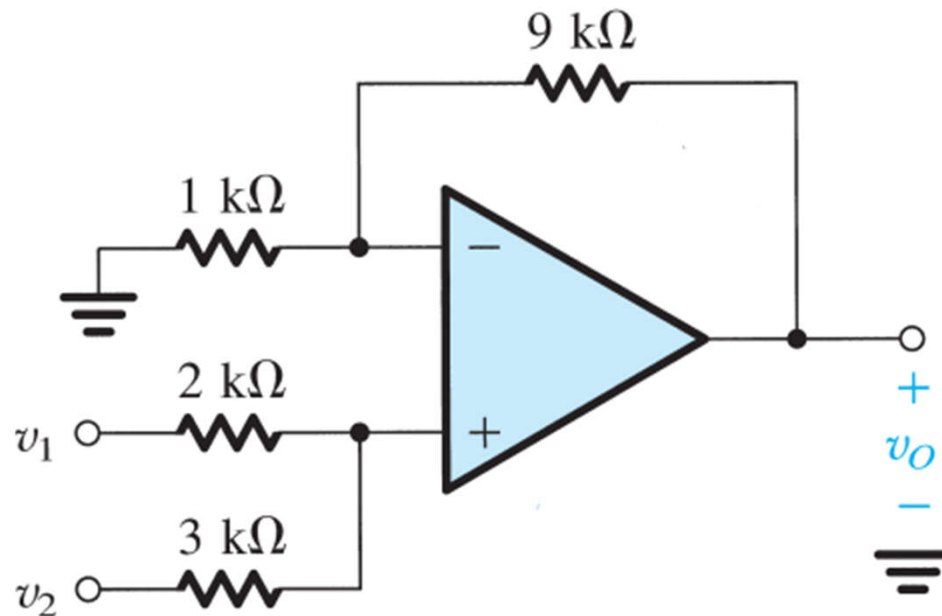


Problem: find  $V_o$

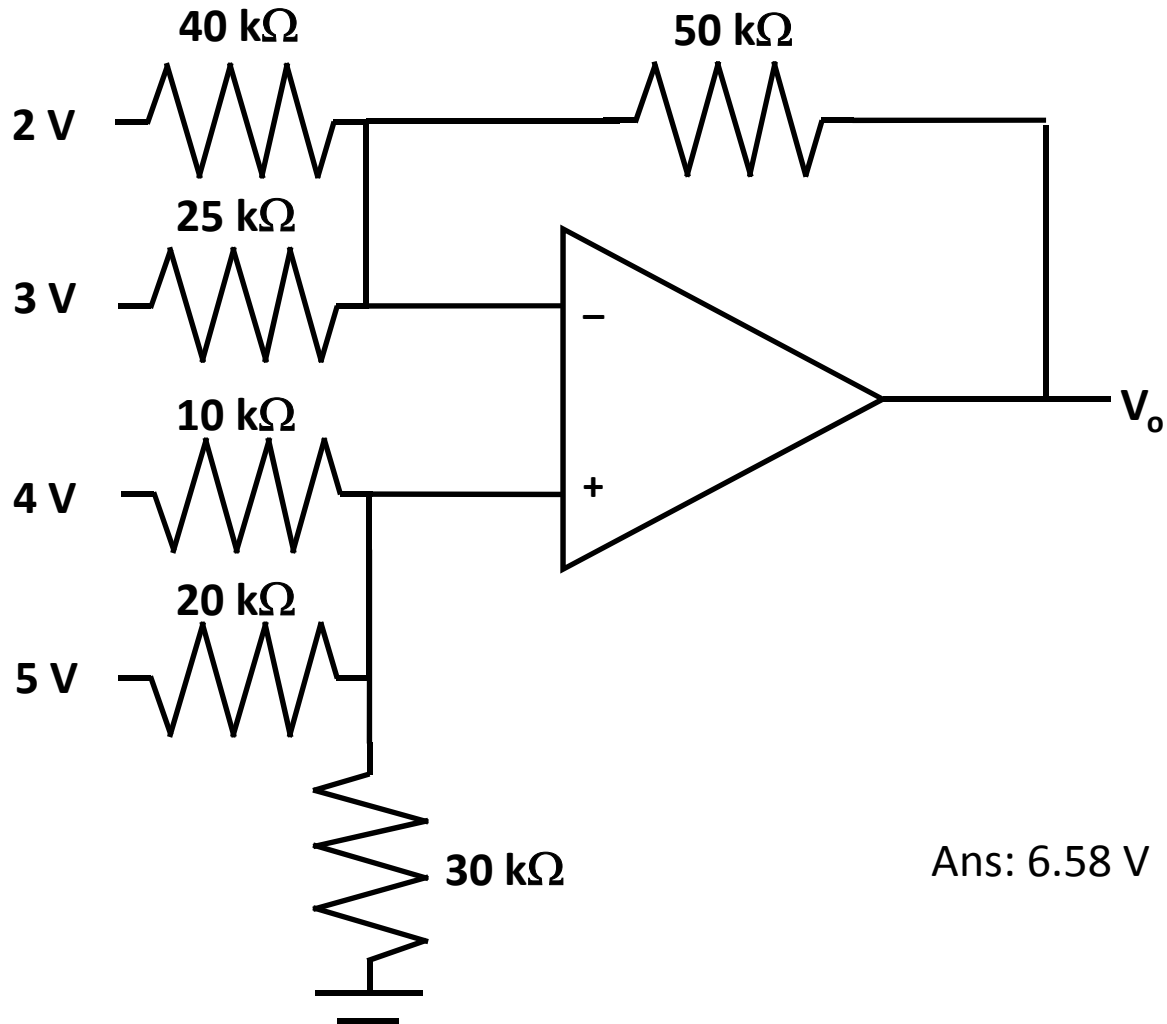

Ans: 6.58 V

- For the circuit in Fig. find the values of  $i_I$ ,  $v_1$ ,  $i_1$ ,  $i_2$ ,  $v_o$ ,  $i_L$ , and  $i_o$ . Also find the voltage gain  $v_o/v_I$ , the current gain  $i_L/i_I$ , and the power gain  $P_L/P_I$

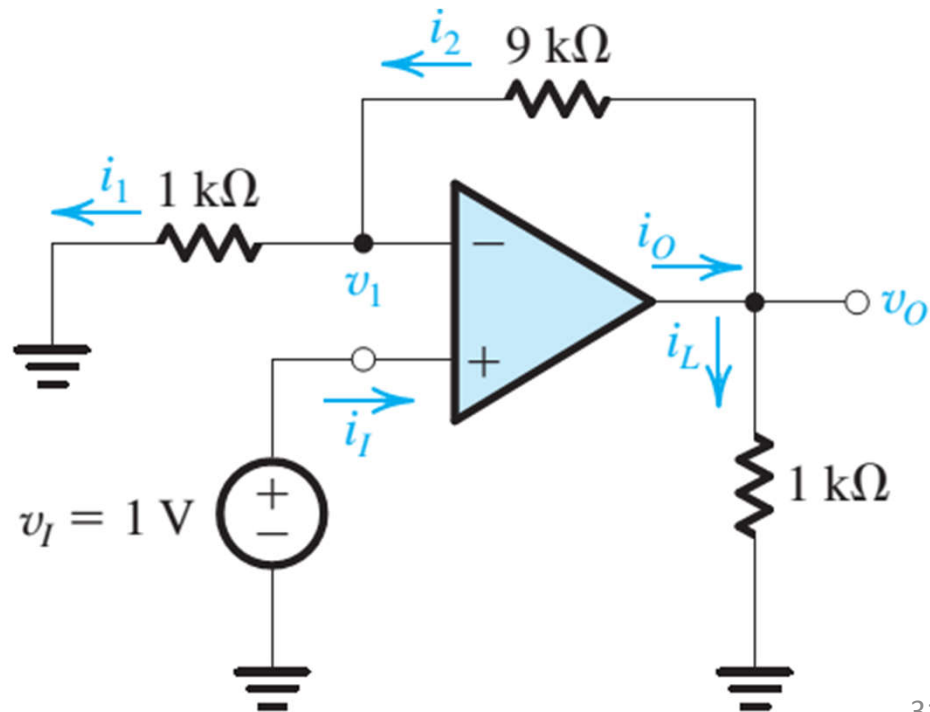0; 1 V; 1 mA; 1 mA; 10  
V; 10 mA; 11 mA; 10  
V/V (20 dB);  $\infty$ ;  $\infty$









# Assignment B.1


(1)

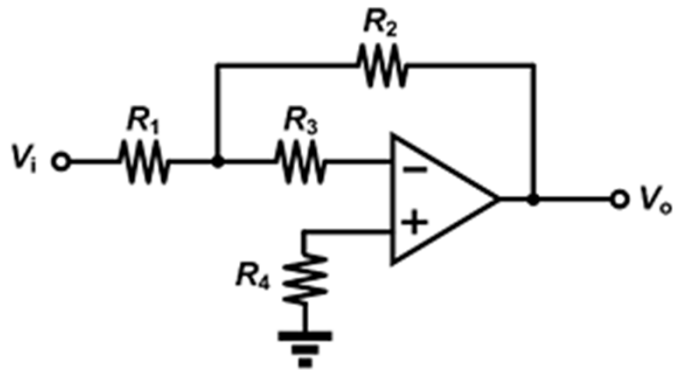

(2)

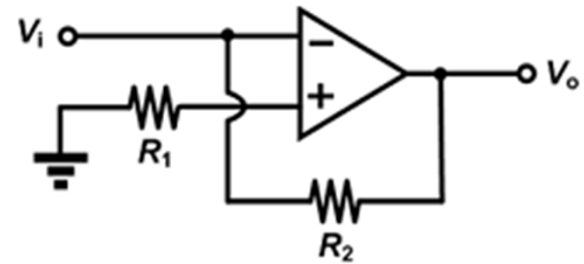


(3)

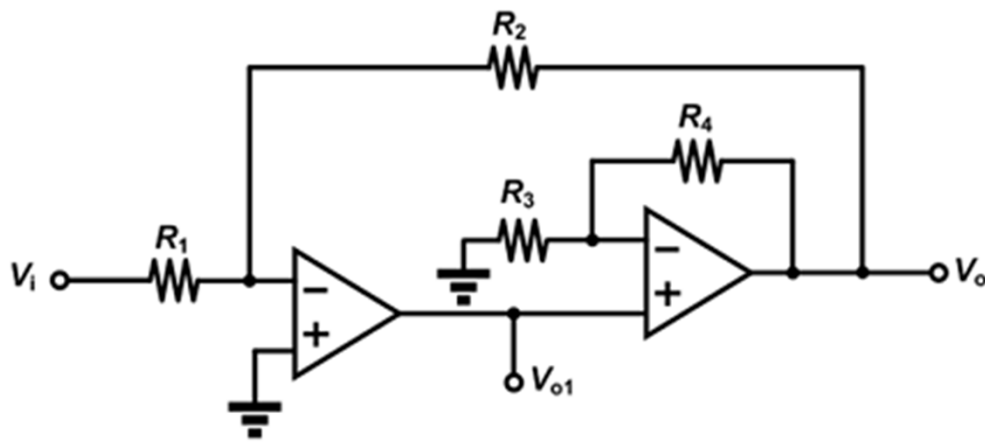


# Assignment B.1

(4)

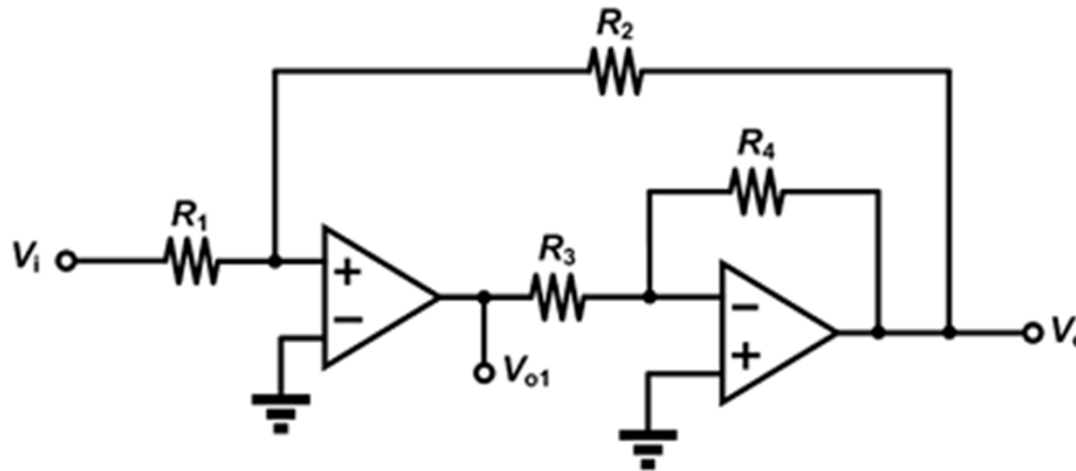
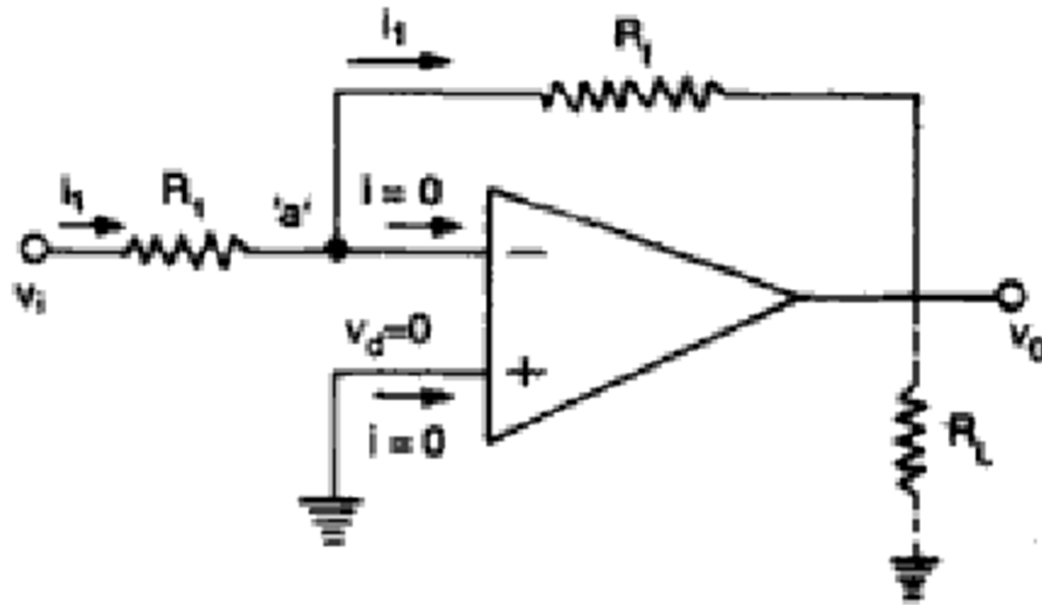
## Assignment B.2

- $R_1 = 10 \text{ k}\Omega$ ,  $R_f = 100 \text{ k}\Omega$ ,  $v_i = 1 \text{ V}$ . A load of  $25 \text{ k}\Omega$  is connected to the output terminal. Calculate (1)  $i_1$  (2)  $v_o$  (3)  $i_L$  and (4) total current  $i_o$  into the output pin.



# Differentiator

Current flowing through capacitor


$$i_C = C \frac{d}{dt}(v_i - v_N) = C \frac{dv_i}{dt}$$

Nodal equation at N

$$C \frac{dv_i}{dt} + \frac{v_o}{R_F} = 0$$

*Solving*

$$v_o = -R_F C \frac{dv_i}{dt}$$

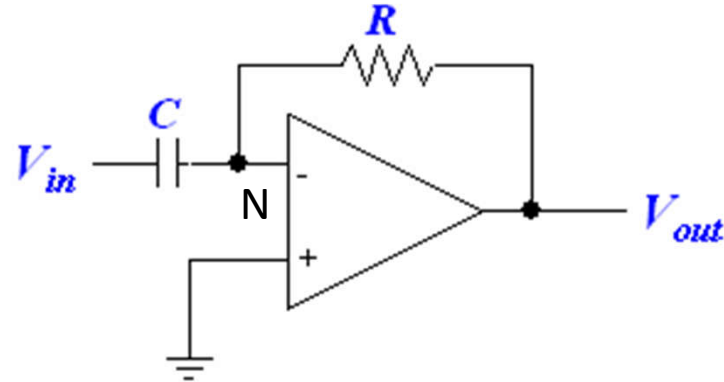

# Integrator


Nodal equation at N

$$\frac{v_i}{R_1} + C_F \frac{dv_o}{dt} = 0$$

$$\frac{dv_o}{dt} = -\frac{1}{R_1 C_F} v_i$$

*Integrating on both sides*
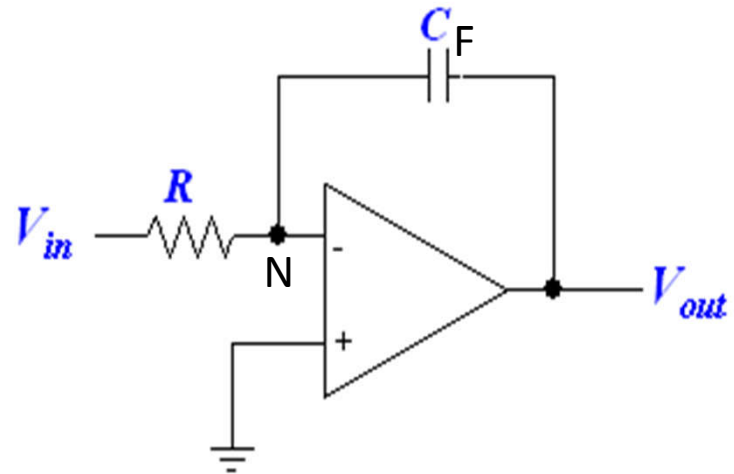
$$v_o = -\frac{1}{R_1 C_F} \int_0^t v_i(t) dt$$




# AC amplifier

- Inverting
- Non-inverting
- To get frequency response

$$V_o = -IR_f = \frac{V_i}{R_1 + \frac{1}{sC}} R_f$$

$$A_{CL} = \frac{V_o}{V_i} = -\frac{R_f}{R_1} \frac{s}{s + \frac{1}{R_1 C}}$$

$$s = j\omega$$

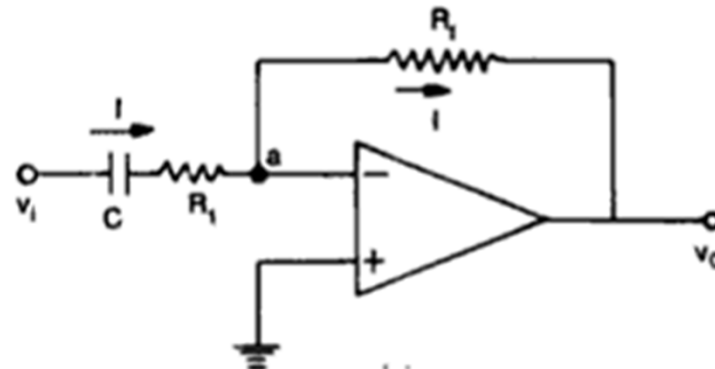

# **Voltage to current converter**

## **Transconductance amplifier**

- Floating load
- Grounded load

# Voltage to current converter


## Transconductance amplifier

- Floating load

$$V_{IN} = i_{IN} R$$

$$i_{IN} = \frac{V_{IN}}{R}$$

$$i_L = i_{IN} = \frac{V_{IN}}{R}$$

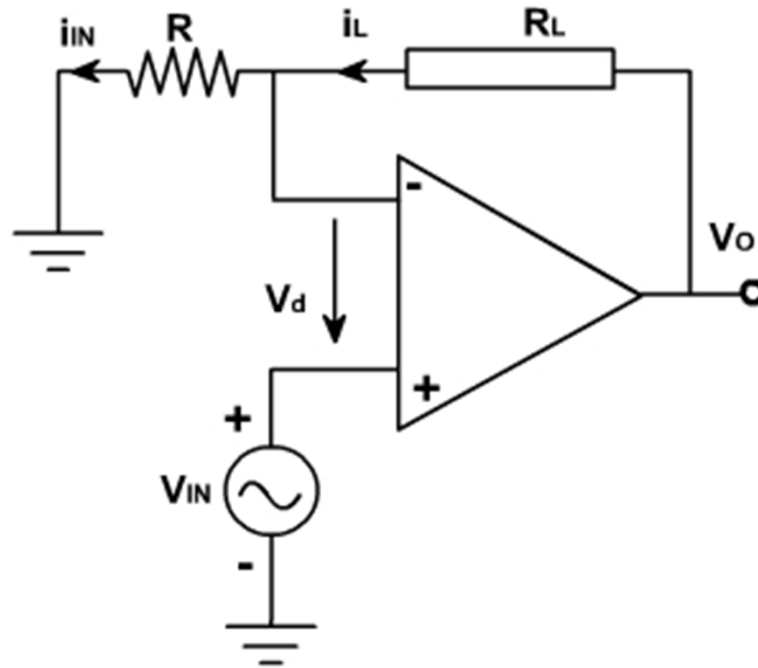




# Voltage to current converter

## Transconductance amplifier

- Grounded load

$$V_2 = V_{IN}$$

$$I_{OUT} = \frac{V_{CC} - V_{IN}}{R}$$

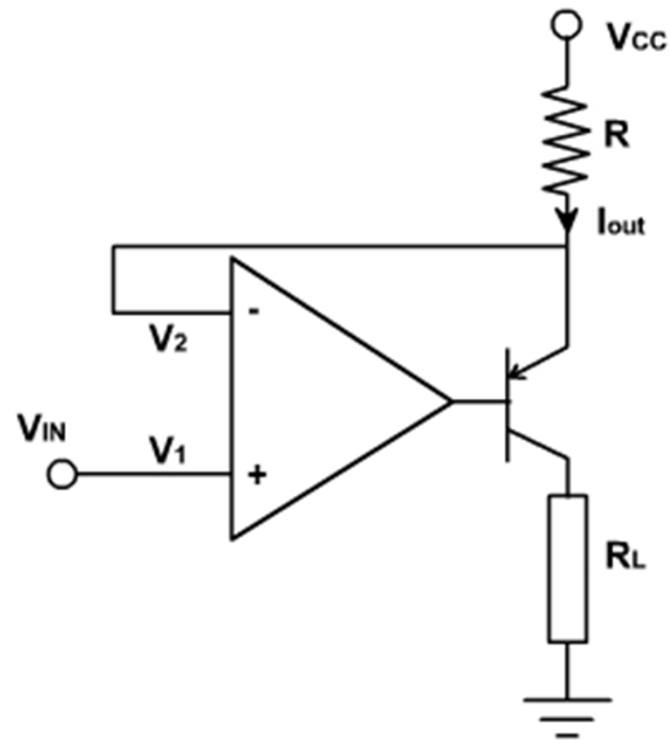

# Voltage to current converter

## Transconductance amplifier

- Grounded load

$$i_1 + i_2 = i_L$$

$$\frac{v_i - v_1}{R} + \frac{v_o - v_1}{R} = i_L$$

$$v_1 = \frac{v_i + v_o - i_L R}{2} \quad (1)$$


*Non-inverting op-amp*

$$v_o = \left[ 1 + \frac{R}{R} \right] v_1 = 2v_1 \quad (2)$$

*From Eqns.(1) & (2)*


$$v_i - i_L R = 0$$

$$i_L = \frac{v_i}{R}$$

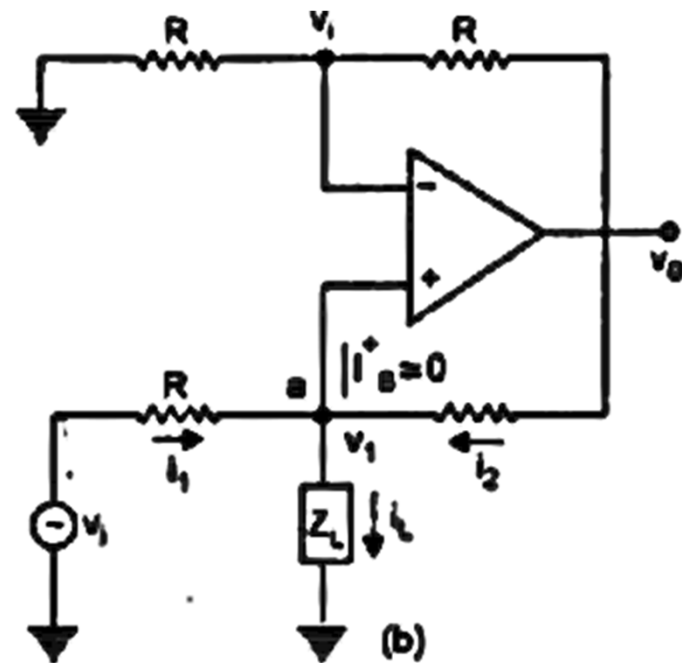
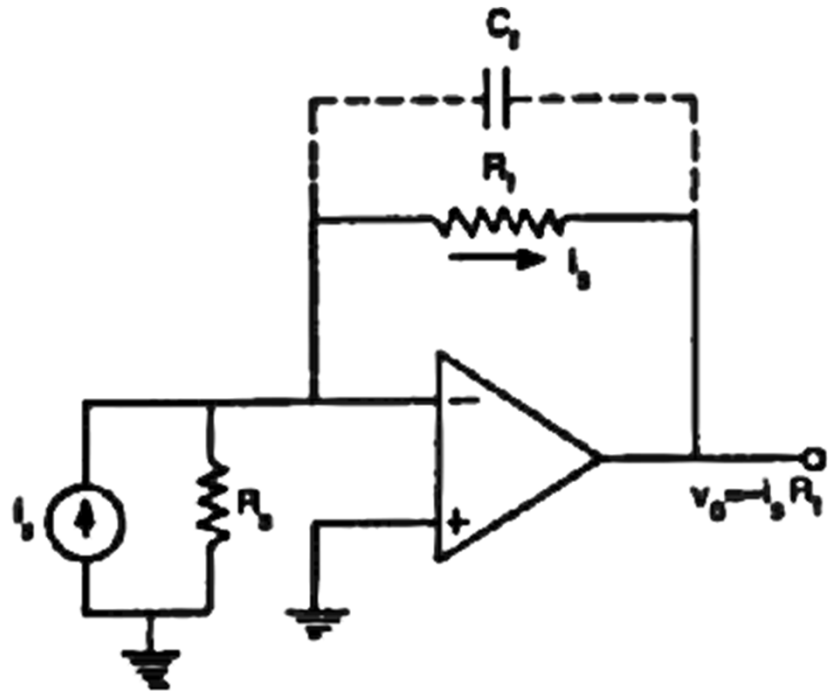
# Current to voltage converter (Transresistance amplifier)

- The output current (proportional to incident radiant energy or light) of a photocell, photodiode and photovoltaic cell can be converted into voltage
- Capacitor serves as filter





$$v_o = -i_s R_f$$

# Op-amp circuits using diodes

- Half-wave rectifier
- Full-wave rectifier
- Peak-value detector
- Clipper
- Clamper


# Half-wave rectifier

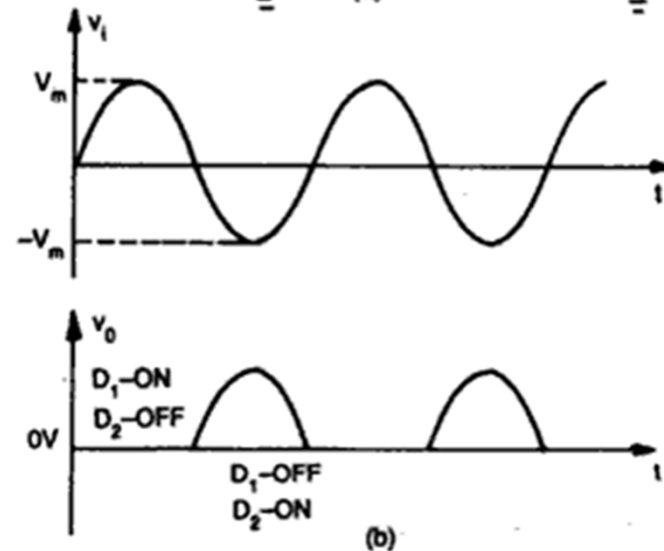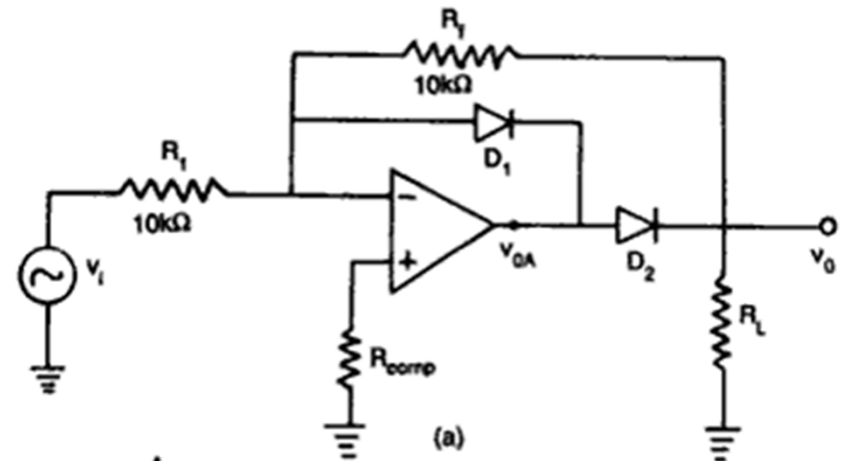

(a) Half-wave rectifier (b) waveforms


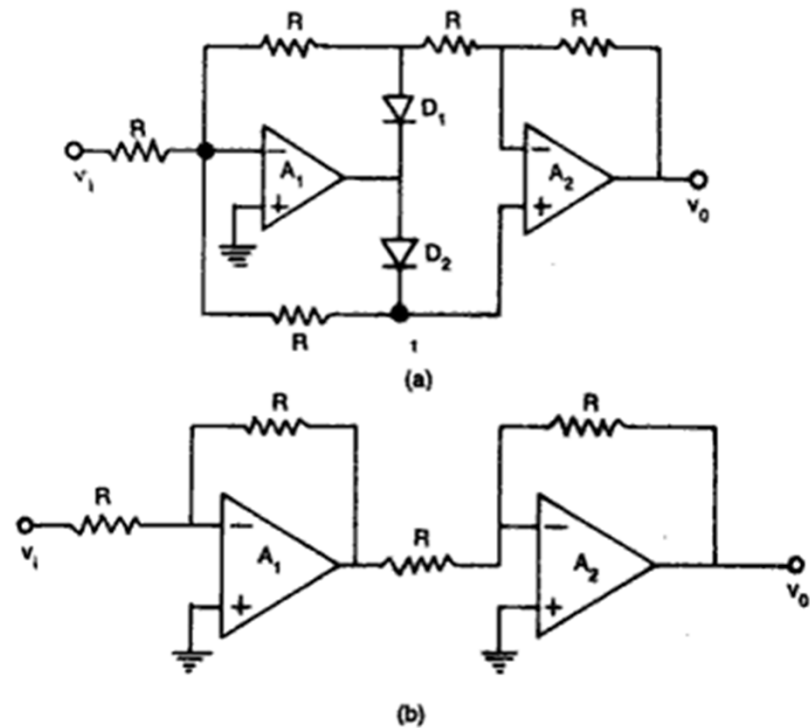
# Full-wave rectifier

- When  $v_i > 0$ , (positive half cycle),
  - $D_1$ -ON,  $D_2$ -OFF
  - $v_o = v_i$
- When  $v_i < 0$ , (negative half cycle),
  - $D_1$ -OFF,  $D_2$ -ON
  - $v_o = v_i$



(a) Full-wave rectifier and (b) its equivalent circuit when  $V_i > 0$

# Peak detector




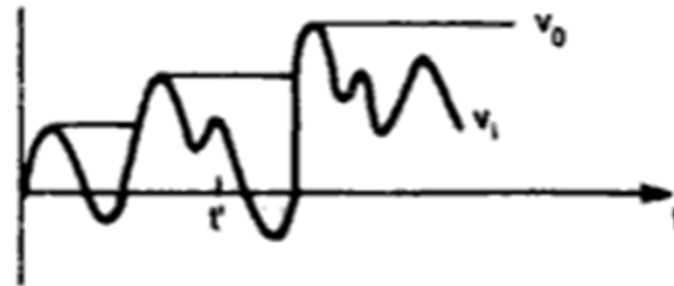
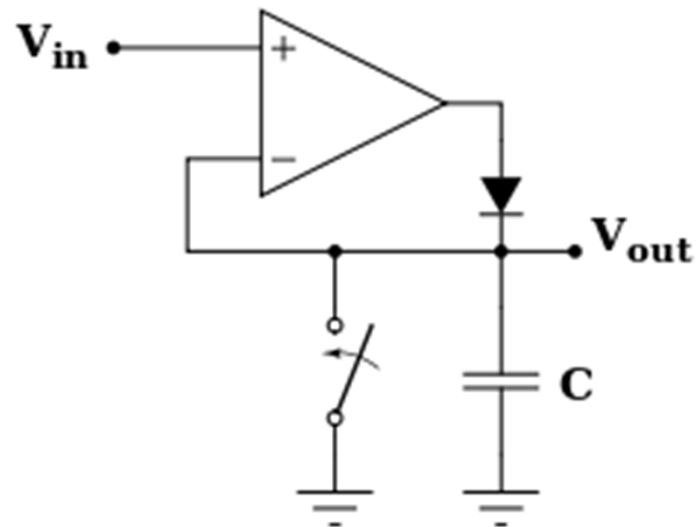


# Clipper

- Positive clipper
  - Positive reference
  - Negative reference
- Negative clipper
  - Positive reference
  - Negative reference








# Positive clipper

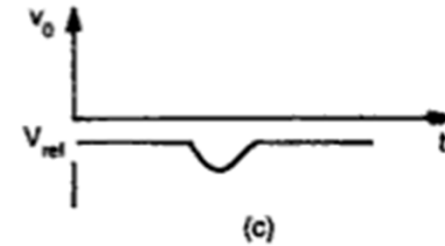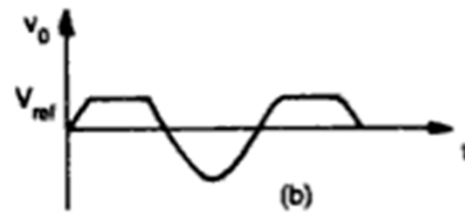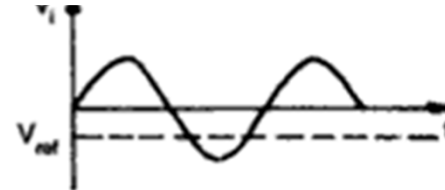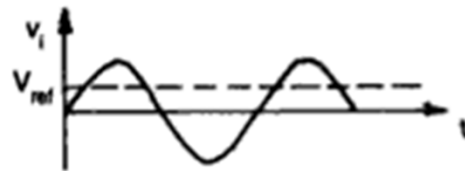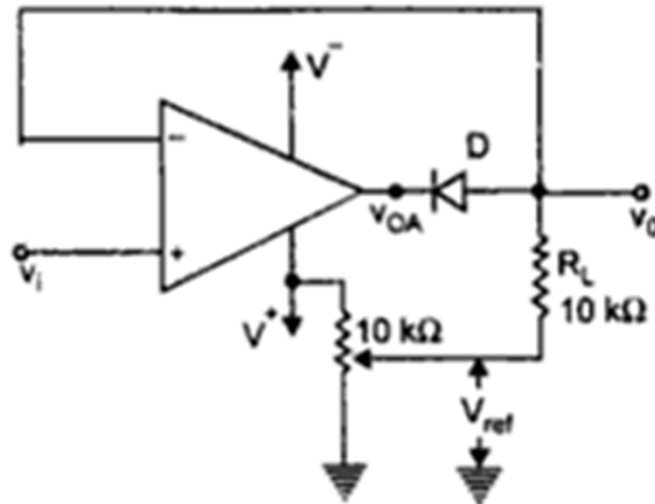

Positive reference

Negative reference




# Negative clipper

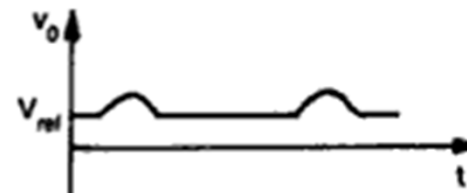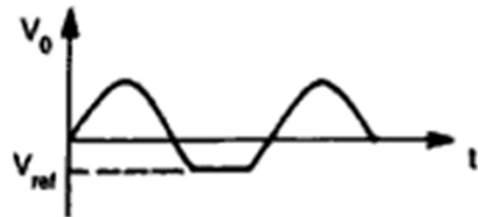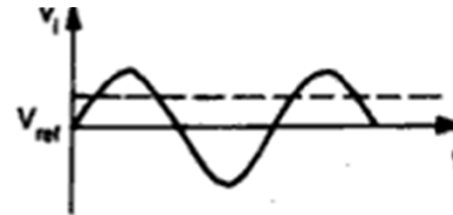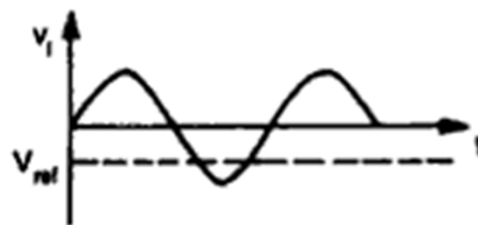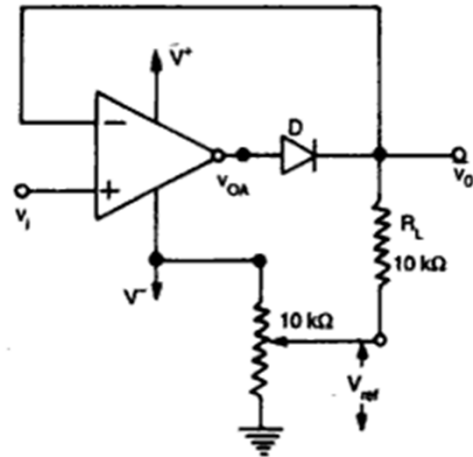

Negative reference


Positive reference

# Clamper

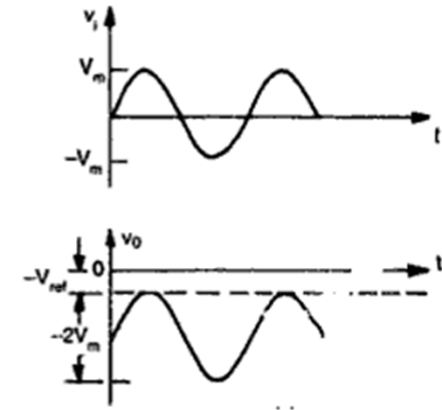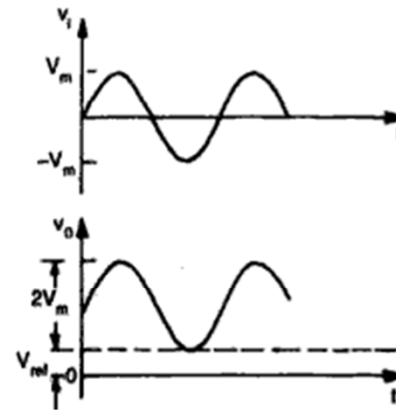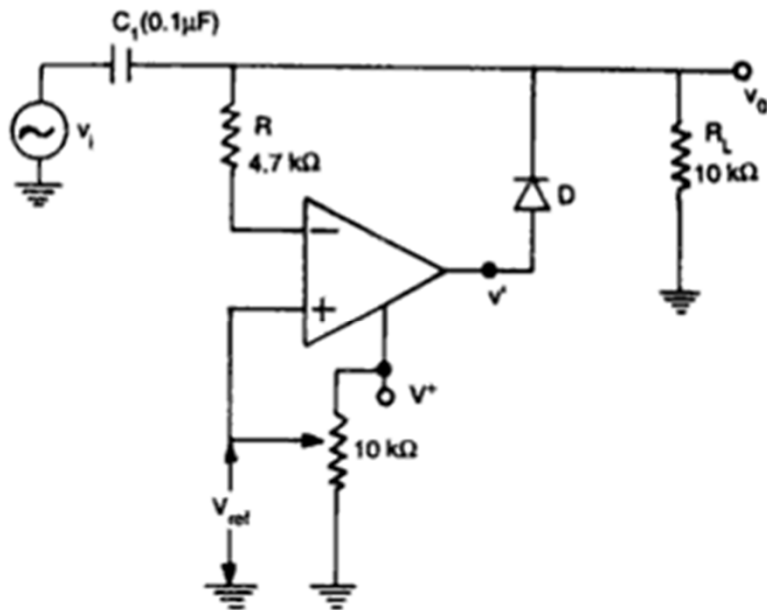


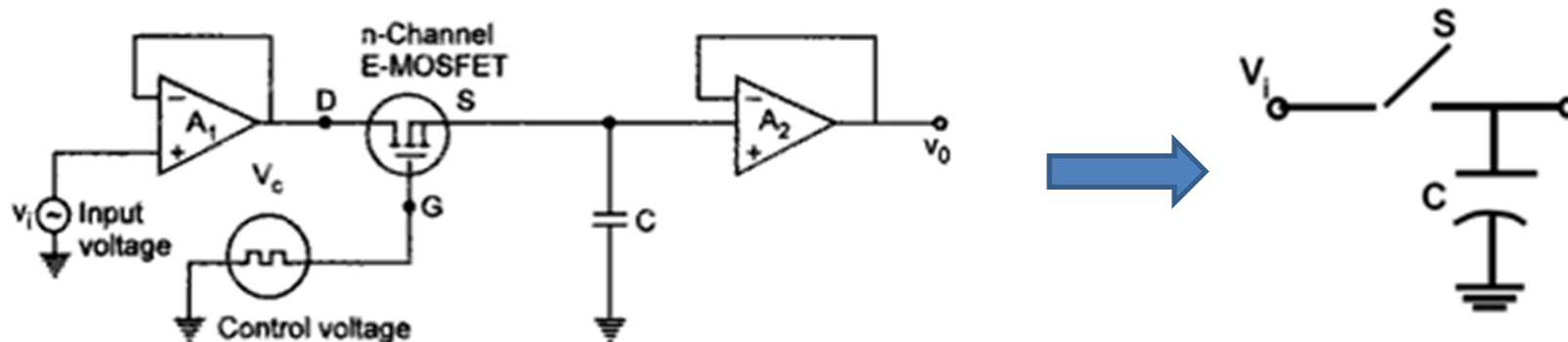
# Sample and hold circuit

- **Signal** to be sampled is applied to drain of the MOSFET
- **Control voltage** given to the gate of the MOSFET


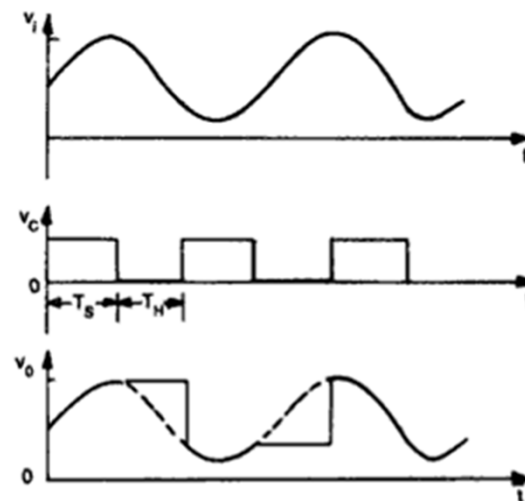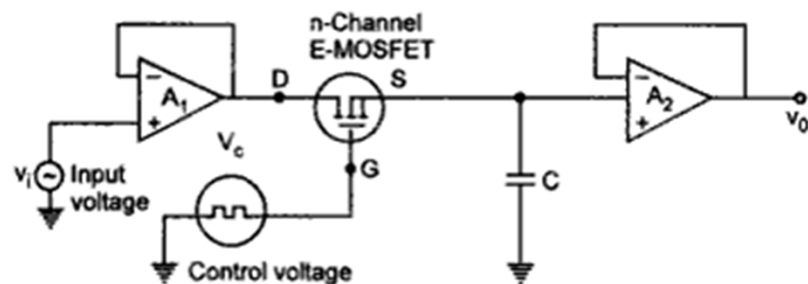
# Sample and hold circuit

- $V_c + V_e$ , MOSFET – ON, Capacitor charges to  $v_i$  (ON time)  $\rightarrow V_o$
- $V_c = 0$  V, MOSFET is OFF, Capacitor cannot discharge through  $A_2$  (High impedance of  $A_2$ ), Capacitor holds the value  $\rightarrow V_o$



# Log amplifier

$$I_E = I_S \left( e^{\frac{qV_E}{kT}} - 1 \right)$$

Base is grounded,


$$\therefore I_C = I_E = I_S \left( e^{\frac{qV_E}{kT}} - 1 \right)$$

$$e^{\frac{qV_E}{kT}} = \frac{I_C}{I_S} + 1$$

$$e^{\frac{qV_E}{kT}} \approx \frac{I_C}{I_S}$$

Take natural log on both sides
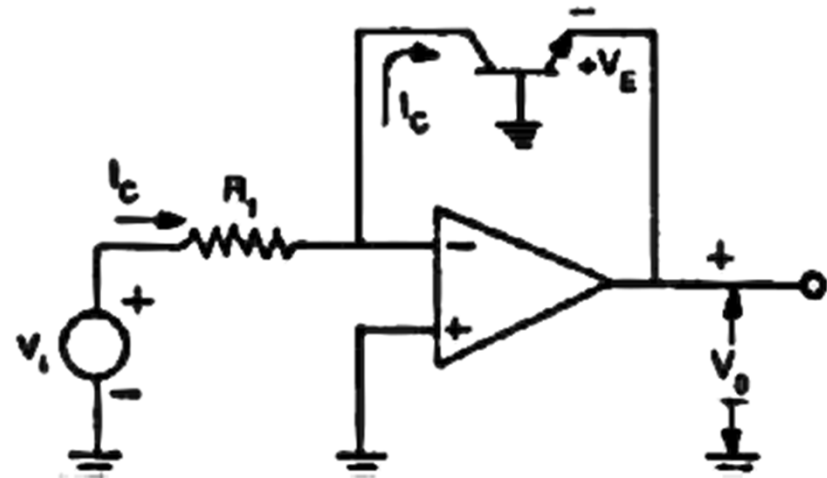
$$V_E = \frac{kT}{q} \ln \left( \frac{I_C}{I_S} \right)$$




Also,

$$V_E = -V_o$$



$$I_C = \frac{V_i}{R_1}$$

$$\therefore V_o = -\frac{kT}{q} \ln \left( \frac{V_i}{I_S R_1} \right)$$

# Antilog amplifier

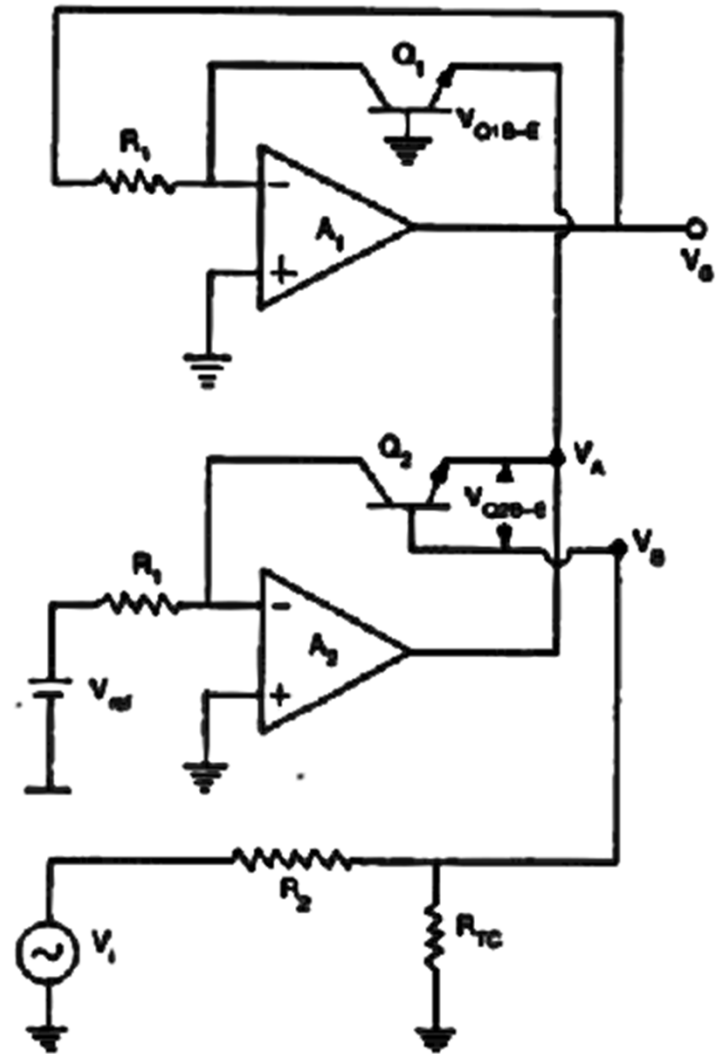

# Transfer characteristics of op-amp

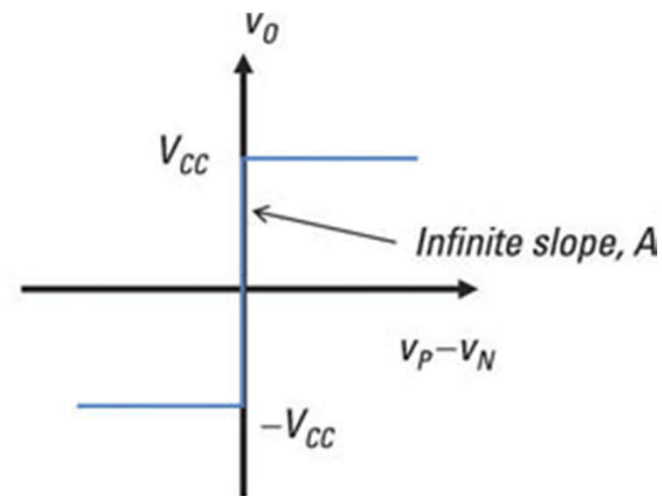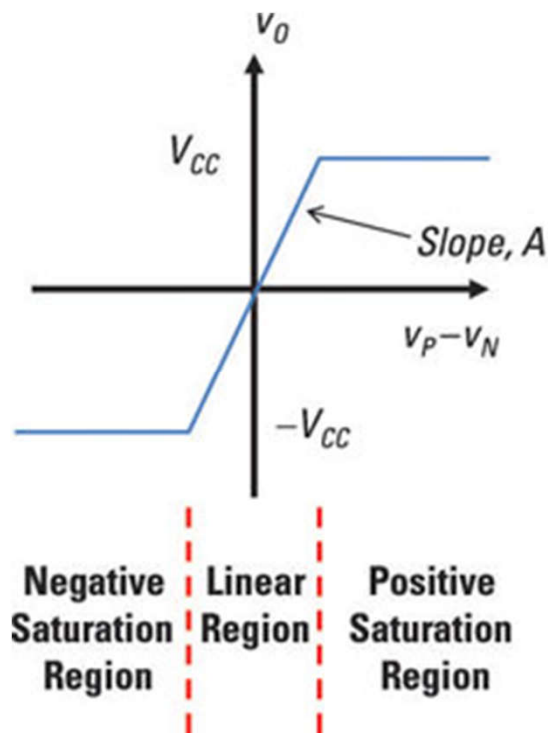

Transfer Characteristic of an Ideal Op Amp

Negative saturated region:	$v_O = -V_{CC}$	$A_v(v_p - v_N) < -V_{CC}$
Linear active region:	$v_O = A_v(v_p - v_N)$	$-V_{CC} < A_v(v_p - v_N) < +V_{CC}$
Positive saturated region:	$v_O = +V_{CC}$	$A_v(v_p - v_N) > +V_{CC}$



# Comparators and waveform generators

- Op-amp in open loop
  - Operates in non-linear fashion
- Open loop applications of op-amp
  - Comparators
  - Detectors
  - Converters etc.

# Comparator

- An analog comparator has

- **Two inputs**


- A constant reference voltage  $V_R$  and other is a
    - Time varying signal  $v_i$

- **One output**  $v_o$

$$v_o = -V_{sat} \quad \text{if } v_i > V_R$$

$$v_o = +V_{sat} \quad \text{if } v_i < V_R$$

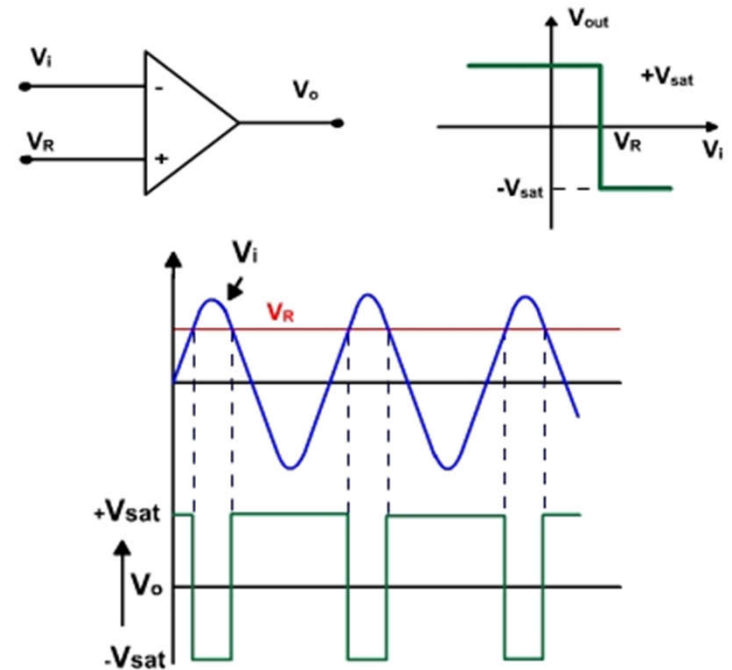**NO feedback**  
**Inverting comparator**




# Non-inverting comparator


# Applications of comparator

- Zero crossing detector
- Window detector


# Zero crossing detector

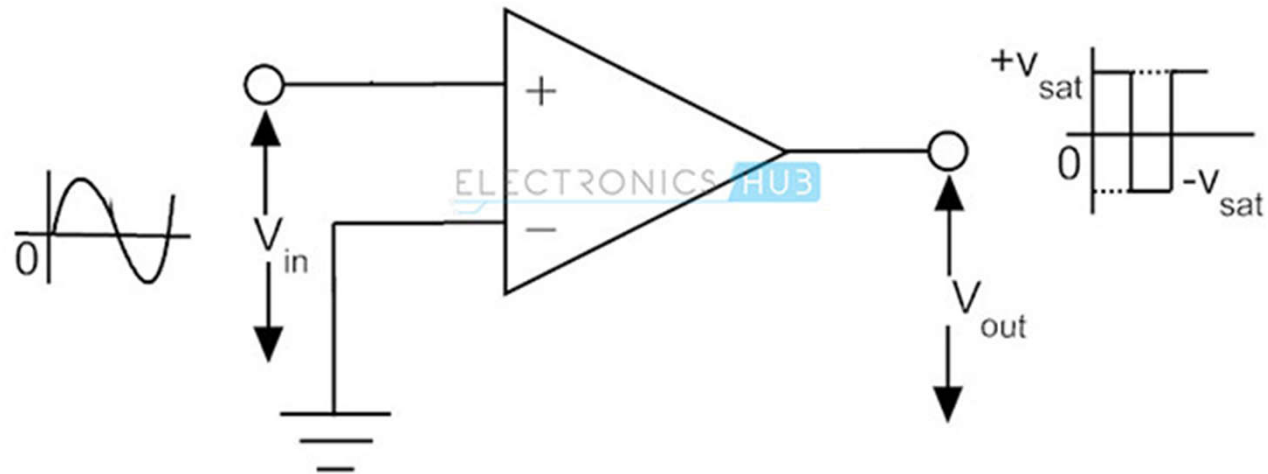

# Window detector

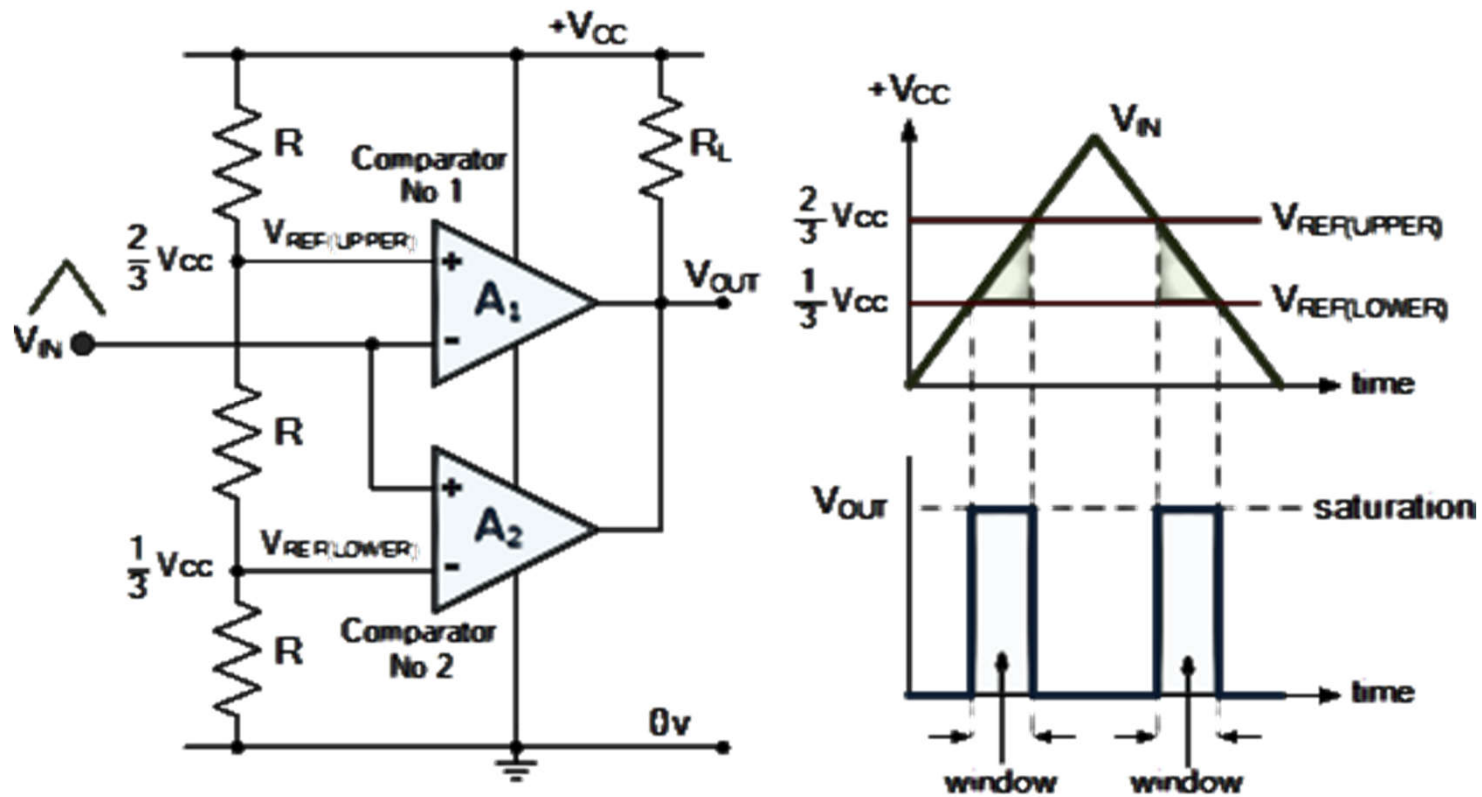


# Three level comparator with LED

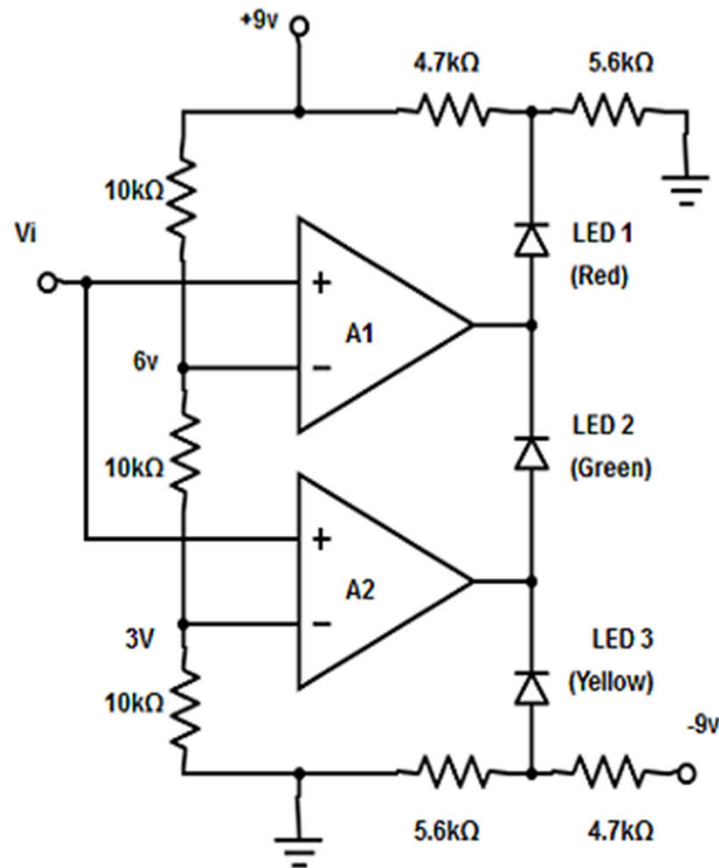

Input (V)	LED 3	LED 2	LED 1
$< 3$			
$3 < v_i < 6$			
$> 6$			
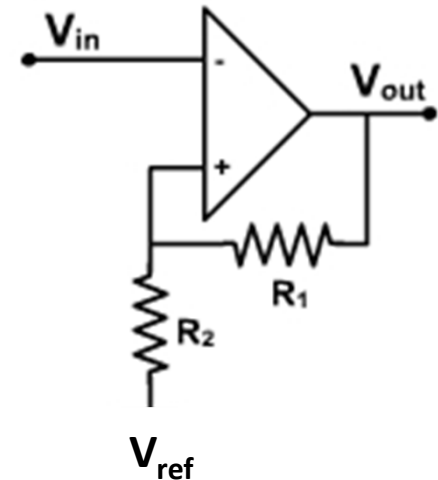
# Regenerative comparator (Schmitt trigger)

- Input is given to inverting terminal
- Feedback voltage is given to non-inverting terminal
- Input triggers output every time it exceeds certain voltage levels
- The voltage levels are
  - Upper threshold voltage ( $V_{UT}$ )
  - Lower threshold voltage ( $V_{LT}$ )





# Regenerative comparator (Schmitt trigger)

- Let,  $v_{out} = +V_{sat}$

Then, voltage at non-inverting terminal is


$$V_{UT} = \frac{R_1}{R_1 + R_2} V_{ref} + \frac{R_2}{R_1 + R_2} V_{sat}$$

As long as  $V_{in} < V_{UT}$ ,  $V_{out} = V_{sat}$


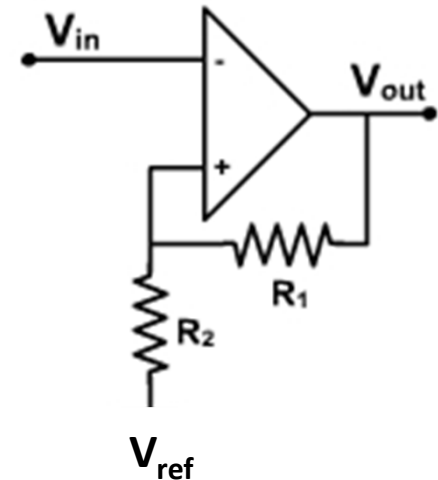
**If  $V_{in}$  is just greater than  $V_{UT}$ ,  $v_{out} = -V_{sat}$**

Then, voltage at non-inverting terminal is

$$V_{LT} = \frac{R_1}{R_1 + R_2} V_{ref} - \frac{R_2}{R_1 + R_2} V_{sat}$$



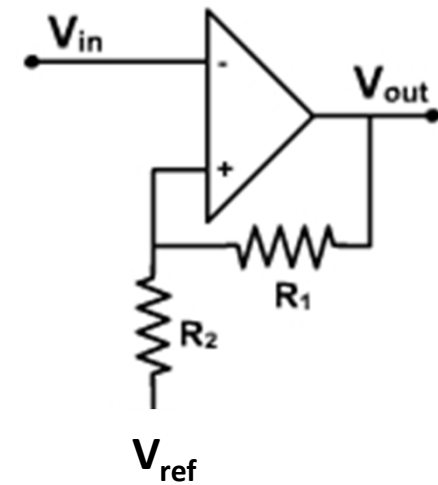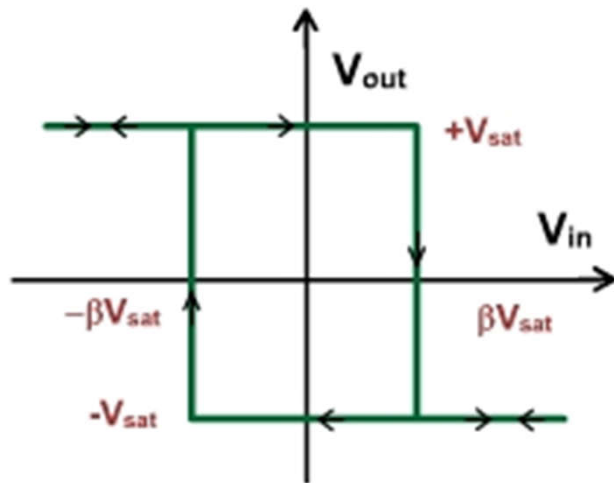
# Regenerative comparator (Schmitt trigger)




The transfer characteristic of Schmitt trigger circuit

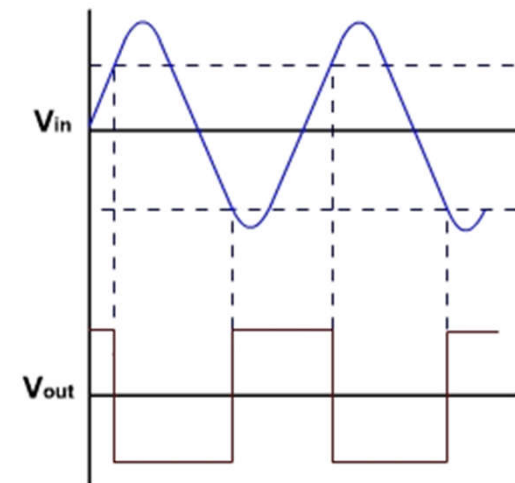If sinusoidal input is given, square wave results


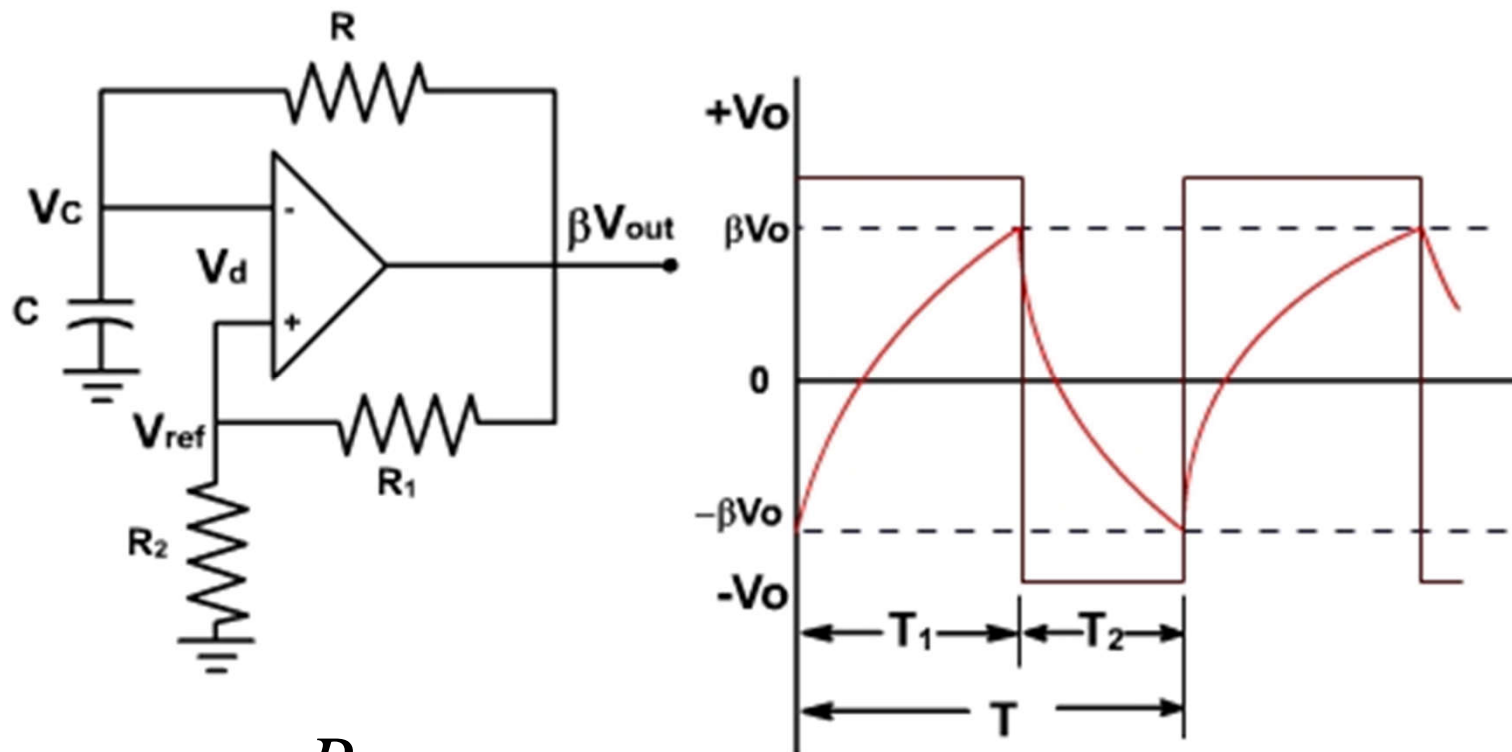
# Square wave generator (Astable multivibrator)



$$\beta = \frac{R_2}{R_1 + R_2}$$

# Square wave generator (Astable multivibrator)

- Let,  $v_o = +V_{sat}$

Voltage across the capacitor

$$v_c(t) = V_f + (V_i - V_f)e^{-t/RC}$$

Final value,  $V_f = +V_{Sat}$

Initial value,  $V_i = -\beta V_{Sat}$

$$\therefore v_c(t) = V_{Sat} - V_{Sat}(1 + \beta)e^{-t/RC}$$


At  $t = T_1$

$$v_c(T_1) = \beta V_{sat}$$


$$\beta V_{sat} = V_{Sat} - V_{Sat}(1 + \beta)e^{-T_1/RC}$$

*Solving*

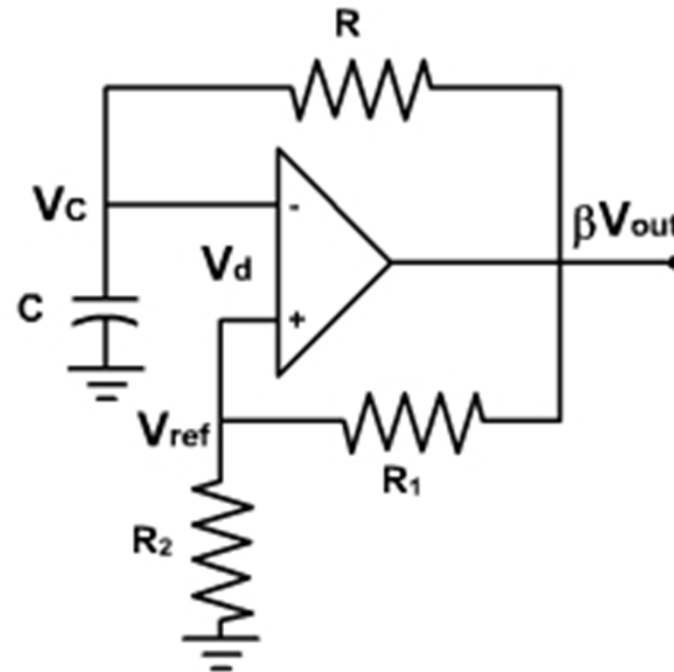
$$T = RC \ln \left( \frac{1 + \beta}{1 - \beta} \right)$$



# Monostable multivibrator

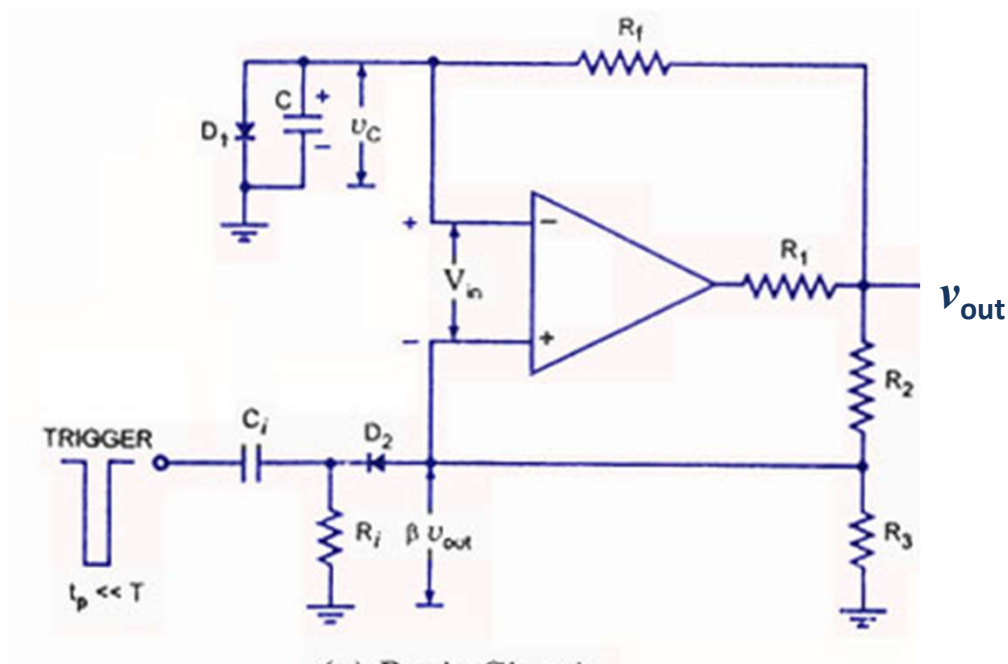

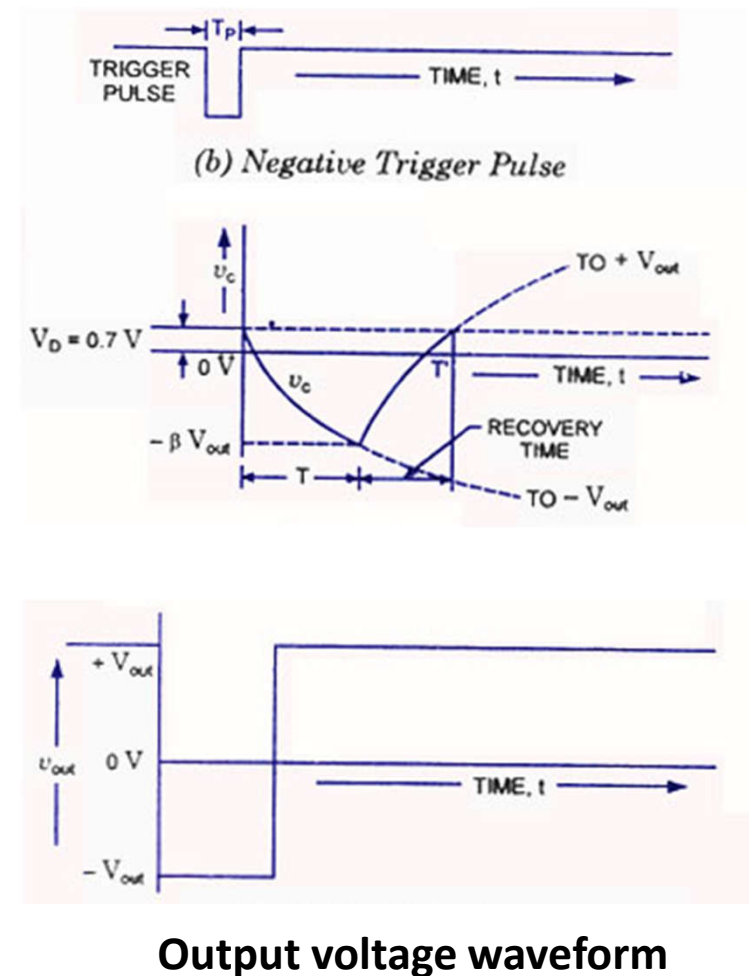- For generating single output pulse whose pulse duration can be varied.
- Requires triggering pulse



# Monostable multivibrator

- Find the gain of the circuit
- Ans: -8

