CO: Computer Organization

Day5

Indian Institute of Information Technology, Sri City

Jan - May - 2018

http://co-iiits.blogspot.in/



Multiplication of Two Integers (unsigned)

Input
$$X = X_3 X_2 X_1 X_0$$

Input $Y = Y_3 Y_2 Y_1 Y_0$

 $Z = X \times Y$, where X is Multiplicand and Y is Multiplier.

$$Z = \sum_{i=0}^{n-1} X.Y_i.2^i = \sum_{i=0}^{n-1} PP_i$$

P	PP_0				$X_3.Y_0$	$X_2.Y_0$	$X_1.Y_0$	$X_0.Y_0$
P	PP_1			$X_3.Y_1$	X_2, Y_1	$X_1.Y_1$	$X_0.Y_1$	
P	PP_2		$X_3.Y_2$	X_2, Y_2	$X_1.Y_2$	$X_0.Y_2$		
F	PP_3	$X_3.Y_3$	$X_2.Y_3$	$X_1.Y_3$	$X_0.Y_3$			

Result $Z = P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0$

Multiplication of Two Integers (unsigned)

Input
$$X = X_3 X_2 X_1 X_0$$

Input $Y = Y_3 Y_2 Y_1 Y_0$

 $Z = X \times Y$, where X is Multiplicand and Y is Multiplier.

$$Z = \sum_{i=0}^{n-1} X.Y_i.2^i = \sum_{i=0}^{n-1} PP_i$$

PP_0	0	0	0	$X_3.Y_0$	$X_2.Y_0$	$X_1.Y_0$	$X_0.Y_0$
PP_1	0	0	$X_3.Y_1$	$X_2.Y_1$	$X_1.Y_1$	$X_0.Y_1$	0
PP_2	0	$X_3.Y_2$	$X_2.Y_2$	$X_1.Y_2$	$X_0.Y_2$	0	0
PP_3	$X_3.Y_3$	$X_2.Y_3$	$X_1.Y_3$	$X_0.Y_3$	0	0	0

Result $Z = P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0$

Multiplication of Two Integers (unsigned)

Ripple-Carry Array Multiplier X₁Y₁ X_0Y_0 X₂Y₀ X_1Y_0 $C_{1,3}$ C_{1,4} FΑ FA FΑ FΑ X3Y2 X₀Y₂ X_2Y_2 C_{2,4} C_{2,3} C_{2,2} C_{2,1} FΑ FΑ FA FA ХзҮз ХоУз X₂Y₃ X₁Y₃ C_{3,4} $C_{3,3}$ C_{3,1} $C_{3,2}$ FA FΑ FA FΑ

All X_i . Y_i s are available at $1\mathcal{T}$.

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
```

All X_i . Y_i s are available at $1\mathcal{T}$. $C_{1,1}$ is available at $3\mathcal{T}$ $C_{1,2}$ is available at $5\mathcal{T}$ $C_{1.3}$ is available at 7T

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
C_{2,2} is available at 9\mathcal{T}
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
C_{2,2} is available at 9\mathcal{T}
C_{2,3} is available at 11\mathcal{T}
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1.1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
C_{2,2} is available at 9\mathcal{T}
C_{2,3} is available at 11\mathcal{T}
C_{2,4} is available at 13\mathcal{T}
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1.1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
C_{2,2} is available at 9\mathcal{T}
C_{2,3} is available at 11\mathcal{T}
C_{2,4} is available at 13\mathcal{T}
C_{3,1} is available at 11\mathcal{T}
```

ICS-110

4 / 15

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
C_{2,2} is available at 9\mathcal{T}
C_{2,3} is available at 11\mathcal{T}
C_{2,4} is available at 13\mathcal{T}
C_{3,1} is available at 11\mathcal{T}
C_{3,4} is available at 17\mathcal{T}
```

```
All X_i. Y_is are available at 1\mathcal{T}.
C_{1,1} is available at 3\mathcal{T}
C_{1,2} is available at 5\mathcal{T}
C_{1.3} is available at 7T
C_{1.4} is available at 9T
C_{2,1} is available at 7T
C_{2,2} is available at 9\mathcal{T}
C_{2,3} is available at 11\mathcal{T}
C_{2,4} is available at 13\mathcal{T}
C_{3,1} is available at 11\mathcal{T}
C_{3,4} is available at 17\mathcal{T}
Condition for Overflow(OF):?
Write the generalized formula for total time:?
```

Multiplication of Two Signed Integers

Input
$$X = X_3 X_2 X_1 X_0$$

Input $Y = Y_3 Y_2 Y_1 Y_0$
 $Z = X \times Y$, where X is Multiplicand and Y is Multiplier.
 $Z = -X.Y_{n-1}.2^{n-1} + \sum_{i=0}^{n-2} X.Y_i.2^i = -PP_{n-1} + \sum_{i=0}^{n-2} PP_i$
Represent each PP using '2n' bits.

$X_3.Y_0$	$X_3.Y_0$	$X_3.Y_0$	$X_3. Y_0$	$X_3. Y_0$	$X_2.Y_0$	$X_1.Y_0$	$X_0.Y_0$
$X_3.Y_1$	$X_3.Y_1$	$X_3.Y_1$	$X_3. Y_1$	$X_2. Y_1$	$X_1.Y_1$	$X_0.Y_1$	
$X_3.Y_2$	$X_3.Y_2$	$X_3.Y_2$	$X_2.Y_2$	$X_1. Y_2$	$X_0.Y_2$		
$\overline{X_3.Y_3}$	$\overline{X_3.Y_3}$	$\overline{X_2.Y_3}$	$\overline{X_1.Y_3}$	$\overline{X_0.Y_3}$			
				1			

Try with example: If X = 1110 = -2 and Y = 1101 = -3, then X.Y = 6.

◆ロト ◆団 ト ◆ 差 ト ◆ 差 ・ 夕 Q ○

Multiplication of Two Signed Integers

Input
$$X = X_3 X_2 X_1 X_0$$

Input $Y = Y_3 Y_2 Y_1 Y_0$
 $Z = X \times Y$, where X is Multiplicand and Y is Multiplier.
 $Z = -X.Y_{n-1}.2^{n-1} + \sum_{i=0}^{n-2} X.Y_i.2^i = -PP_{n-1} + \sum_{i=0}^{n-2} PP_i$
Represent each PP using '2n' bits.

$X_3.Y_0$	$X_3.Y_0$	$X_3.Y_0$	$X_3.Y_0$	$X_3.Y_0$	$X_2.Y_0$	$X_1.Y_0$	$X_0.Y_0$
$X_3.Y_1$	$X_3.Y_1$	$X_3.Y_1$	$X_3.Y_1$	$X_2.Y_1$	$X_1.Y_1$	$X_0.Y_1$	0
$X_3.Y_2$	$X_3.Y_2$	$X_3.Y_2$	$X_2.Y_2$	$X_1.Y_2$	$X_0.Y_2$	0	0
$\overline{X_3.Y_3}$	$\overline{X_3.Y_3}$	$\overline{X_2.Y_3}$	$\overline{X_1.Y_3}$	$\overline{X_0.Y_3}$	0	0	0
0	0	0	0	1	0	0	0

Try with example: If X = 1110 = -2 and Y = 1101 = -3, then X.Y = 6.

←□▶ ←□▶ ← □ ▶

Multiplication of Two Signed Integers


Draw a Combinational Array Multiplier or Ripple-Carry Array Multiplier.

Write the generalized formula for total time:?

Carry Save Adder (CSA)

Input $A = A_3 A_2 A_1 A_0$ Input $B = B_3 B_2 B_1 B_0$ Input $C = C_3 C_2 C_1 C_0$

4 Bit Carry Save Adder

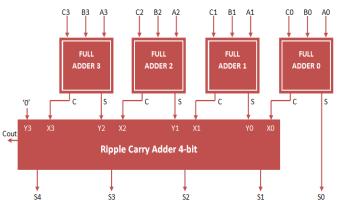


How to perform the addition of 4-inputs(A, B, C, D) using CSAs

Carry Save Adder (CSA)

Input $A = A_3 A_2 A_1 A_0$ Input $B = B_3 B_2 B_1 B_0$ Input $C = C_3 C_2 C_1 C_0$

4 Bit Carry Save Adder

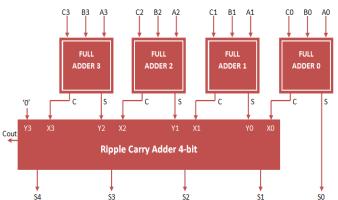


How to perform the addition of 4-inputs(A, B, C, D) using CSAs.

Carry Save Adder (CSA) for 4 inputs

Input $A = A_3 A_2 A_1 A_0$ Input $B = B_3 B_2 B_1 B_0$ Input $C = C_3 C_2 C_1 C_0$ Input $D = D_3 D_2 D_1 D_0$

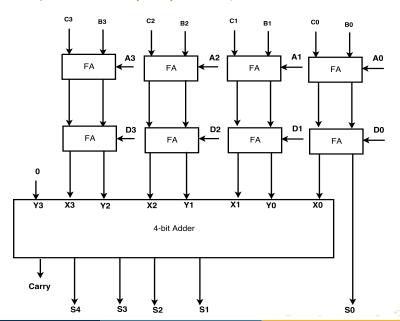Carry Save Adder (CSA) for 4 inputs. is it correct!



Multiplication of Two Integers using CSAs

Input $M=m_3m_2m_1m_0$ Input $Q=q_3q_2q_1q_0$ $Z=M\times Q$, where M is Multiplicand and Q is Multiplier. $Z=\sum_{i=0}^{n-1}M.q_i.2^i=\sum_{i=0}^{n-1}PP_i$ Here PPs are summands.

Try with example: If M = 1110 = 14 and Q = 1101 = 13, then M.Q = 182.

Multiplication of Two Integers using CSAs

Input $M = m_3 m_2 m_1 m_0$

Input $Q = q_3q_2q_1q_0$

 $P = M \times Q$, where M is Multiplicand and Q is Multiplier.

PP_0	0	0	0	0	$m_3.q_0$	$m_2.q_0$	$m_1.q_0$	$m_0.q_0$
PP_1	0	0	0	$m_3.q_1$	$m_2.q_1$	$m_1.q_1$	$m_0.q_1$	0
PP_2	0	0	$m_3.q_2$	$m_2.q_2$	$m_1.q_2$	$m_0.q_2$	0	0
PP_3	0	m ₃ .q ₃	$m_2.q_3$	$m_1.q_3$	$m_0.q_3$	0	0	0

PP_i stands for parallel product 'i'.

Result $Z = P_7 P_6 P_5 P_4 P_3 P_2 P_1 P_0$

where $P_0 = m_0.q_0$

Multiplication of Two Integers using CSAs Multiplication of Two 4-bit numbers

Level Num	No. of Summands	No. of Groups	Remaining Summands
1	4	1	1
2	3	1	0
3	2	0	0

Time= $1+2\times2+6$ (using 4-bit CLAs)= $11\mathcal{T}$.

Multiplication of Two Integers using CSAs Multiplication of Two 8-bit numbers

Level Num	No. of Summands	No. of Groups	Remaining Summands
1	8	2	2
2	6	2	0
3	4	1	1
4	3	1	0
5	2	0	0

Time= $1+2\times4+10$ (using 4-bit CLAs)= $19\mathcal{T}$.

Multiplication of Two Integers using CSAs

Time= Time to generate PPs+ (2 x No. of levels of CSA)+(Time to perform final addition)

Carry Save Adder (CSA) for 16 inputs

